

# VHDL

---

AnsLab Co.,Ltd.

E-Mail :

*goodkook@nms.anslab.co.kr*

URL:

*http://www.anslab.co.kr*

# Previous Knowledge ...

---

## ■ Digital System

■ Number & Codes

■ Combinatorial Logic (Gates)

■ Sequential Logic (F/F, Registers, Counters, State-Machine)

■ CAD experience (Schematics?)

## ■

■ C ? Pascal ? BASIC ? Fortran ? Cobol ?

■ HDL Language !

■ , HDL

!!!

## ASIC/VHDL

---

ASIC Overview

HDL vs. Programming Language

About PLD : Architecture & Prog.


- 
- Analog : Amplifier
  - Digital : Simple TR. Switch
  - Analog : , Circuit Simulation(SPICE)
  - Digital : , Logic Simulation
  - Analog :  $RC+TR (<10)$
  - Digital : Switching TR. ( $>10M$ )

# Digital

- Transistor Circuit
  - TR Circuit : Full-Custom
- Gate/FlipFlop Cell
  - Cell Library : Semi-Custom (SSI)
- Functional Module
  - Adder, Multiplier, Register, Counter (LSI)
- Processor-Memory
  - Processor, Memory (VLSI)
- System
  - SOC (System-On-Chip)



# Digital

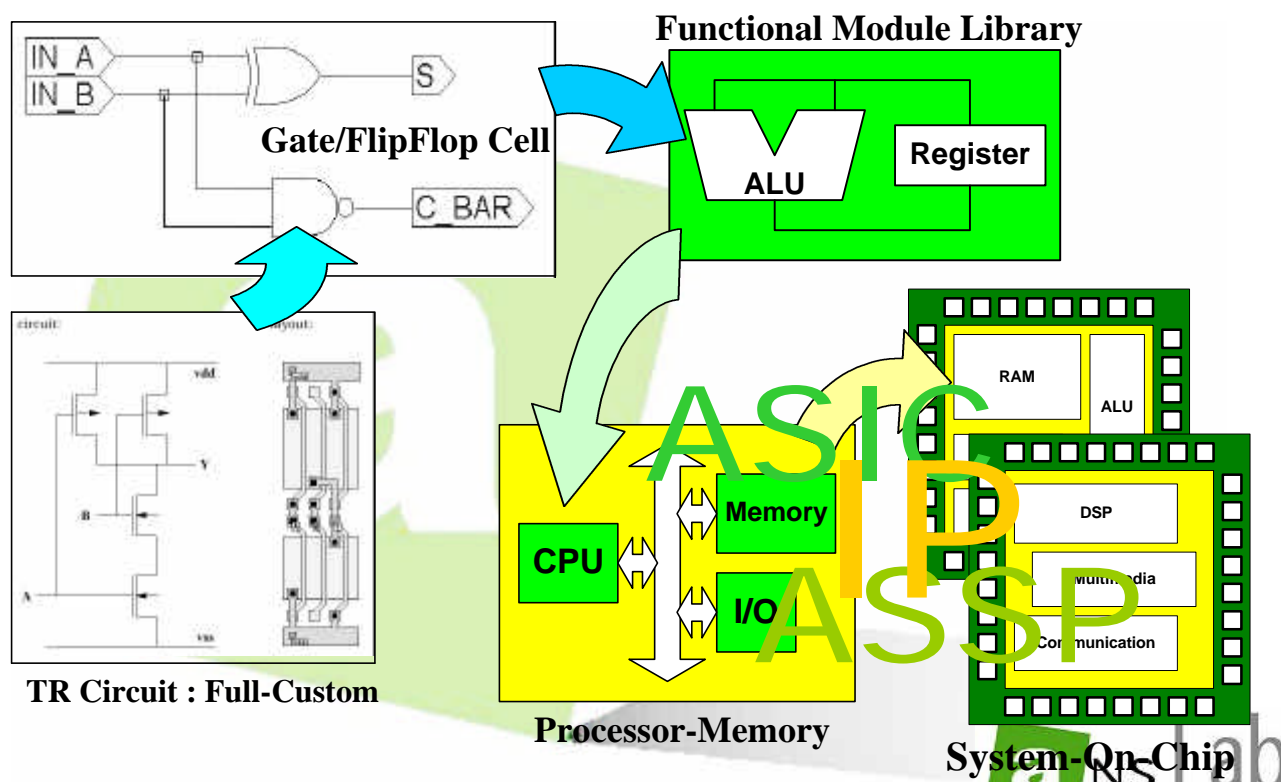

- Transistor Circuit
  - Layout Editor & Circuit/Switch Simulator
- Gate/FlipFlop
  - Schematic Editor & Logic Simulator
- ASIC
  - Hardware Description Language (HDL)
    - Verilog HDL/VHDL
  - HDL & Schematic Mixed



## ASIC

- ASIC
    - Semi-Custom (Standard Cell/Gate-Array)
    - PLD (SPLD/EPLD/CPLD/FPGA)
  - PLD
    - Logic → PAL/GAL → TTL ?
    - CPLD & FPGA → >100K Gate
    - 10,000~50,000 Gate →
- ← Time-To-Market



# HDL

# 가?

“ ”

“ ”가




“ ”



*Easy to Describe Design*  
*Fast Implementation*



## HDL vs. Programming Language

 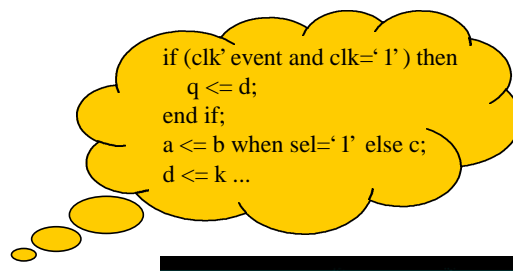 

## HDL : Language ?

### ■ Hardware Description Language

- Statements
  - | Sequential
  - | Concurrent
- Syntax
- Keywords
- Objects
- Operators



## HDL : Hardware Description ?

### ■ Hardware Description Language

Netlist/Dataflow	Behavior/Inference FF
<pre>-- AND Gate a &lt;= b AND c;  -- MUX d &lt;= e when f='1' else g;</pre>	<pre>-- Flip-Flop if rising_edge(clk) then     q &lt;= d; end if;  -- MUX if s='1' then     d &lt;= e; else     d &lt;= f; end if;</pre>



## HDL and Programming Language

	Programming Language	Hardware Language
Purpose	Software (Executable Binaries)	Hardware (Hardwired Logics)
Entry	Text & Visual Tools	
Development	Compile & Link	Compile for Simulation & Synthesis for Hardware
Debugging	Executes & View Result (Text or Graphics)	Simulation & View Waveform
Statement	Sequential Only	Basically Concurrent Sequential for Behavior Description

## HDL : Concurrent & Sequential Statement

### Order of Statements

C Programming Language	Hardware Language
d = a * e; a = b + c;	a <= b OR c; d <= a AND c;
a = b + c; d = a * e;	

### Objects

C Programming Language	Hardware Language
All Registered	Signal Name & Registered

## HDL : Recursive

### Recursive Statements

C Programming Language	Hardware Language (erroneous*)
d = a + c; a = b * d;	d <= a OR c; a <= b AND d;

\* Use Latch or Flip-Flop to be recursive algorithm equiv.

### Latch

Recursive (NO Good*)	Behavior
q <= a NAND q_bar; q_bar <= b NAND q;	if (l='1') then q <= d; end if;

\*\* No real-gates, just equivalent functions on PLD



## HDL : Multiple Drive

### Multiple Drive Error (cause ERC/DRC Violation)

C Programming Language	Hardware Language (Error)
a <= b + c;	a <= b OR c;
...	...
a <= d * e;	a <= d AND e;

### Resolve Multiple Drived Signal

#### Multi-Valued Signal & Resolution Function

- | std\_logic : 9-value { 'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-' }
- | bit : 2-value, { '0', '1' }, NOT RESOLVED





# Multiple Drive

- On Concurrent Assignment, multiple source to one signal must be resolved
- Multiple Drive Problem is common when modeling the buses with three-state drivers
- std\_logic\_1164 provides resolved type and resolution function "resolved".

subtype **std\_logic** is resolved std\_ulogic;




# Resolution Function (IEEE 1164)

```

-----
-- resolution function
-----
CONSTANT resolution_table : stdlogic_table := (
-----
-- | U X 0 1 Z W L H - | |
-----
( 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U', 'U' ), -- | U |
( 'U', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X' ), -- | X |
( 'U', 'X', '0', 'X', '0', '0', '0', '0', 'X', 'X' ), -- | 0 |
( 'U', 'X', 'X', '1', '1', '1', '1', '1', 'X', 'X' ), -- | 1 |
( 'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', 'X', 'X' ), -- | Z |
( 'U', 'X', '0', '1', 'W', 'W', 'W', 'W', 'X', 'X' ), -- | W |
( 'U', 'X', '0', '1', 'L', 'W', 'L', 'W', 'X', 'X' ), -- | L |
( 'U', 'X', '0', '1', 'H', 'W', 'W', 'H', 'X', 'X' ), -- | H |
( 'U', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X', 'X' ) -- | - |
);

FUNCTION resolved ( s : std_ulogic_vector ) RETURN std_ulogic IS
  VARIABLE result : std_ulogic := 'Z';
BEGIN
  IF (s'LENGTH = 1) THEN RETURN s(s'LOW);
  ELSE
    FOR i IN s'RANGE LOOP
      result := resolution_table(result, s(i));
    END LOOP;
  END IF;
  RETURN result;
END resolved;

```

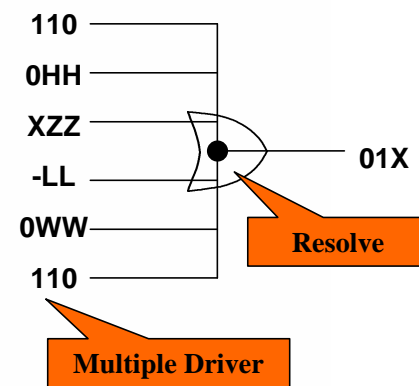

# Resolve Multiple Drive Error

```
entity test_resolver is
  port ( a, b : bit ;
        o : out bit ) ;
end test_resolver ;
architecture dataflow of test_resolver is
  signal tmp : bit ;
begin
  tmp <= a ;
  tmp <= b ;
  o <= tmp ;
end dataflow ;
```

Use resolved type

```
library ieee;
use ieee.std_logic_1164.all;
entity test_resolver is
  port ( a, b : std_logic ;
        o : out std_logic ) ;
end test_resolver ;
architecture dataflow of test_resolver is
  signal tmp : std_logic ;
begin
  tmp <= a ;
  tmp <= b ;
  o <= tmp ;
end dataflow ;
```

write resolution function



```
entity test_resolver is
  port ( a, b : bit ;
        o : out bit ) ;
end test_resolver ;

architecture dataflow of test_resolver is

  -- Write the resolution function that ANDs the elements:
  function my_and_resolved (a : bit_vector) return bit is
    variable result : bit := '1' ;
  begin
    for i in a'range loop
      result := result AND a(i) ;
    end loop ;
    return result ;
  end my_and_resolved ;


  -- Declare the signal and attach the resolution function to it:
  signal tmp : my_and_resolved bit ;
begin
  tmp <= a ;
  tmp <= b ;
  o <= tmp ;
end dataflow ;
```



# HDL vs. Programming Language


## HDL

- Instanciated Unit
- Register Inference

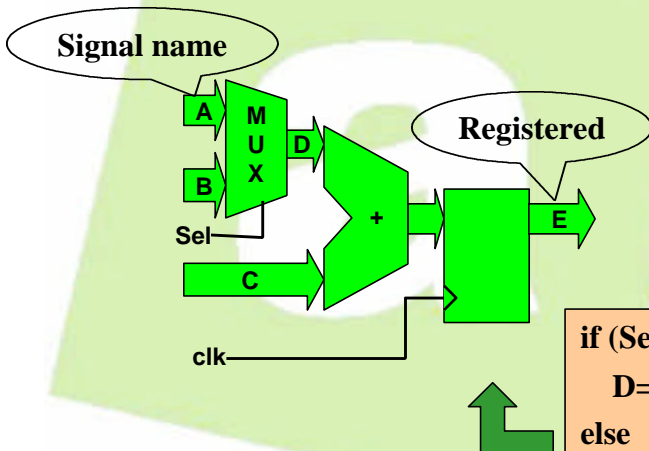

## Programming Language

- Processor-Memory

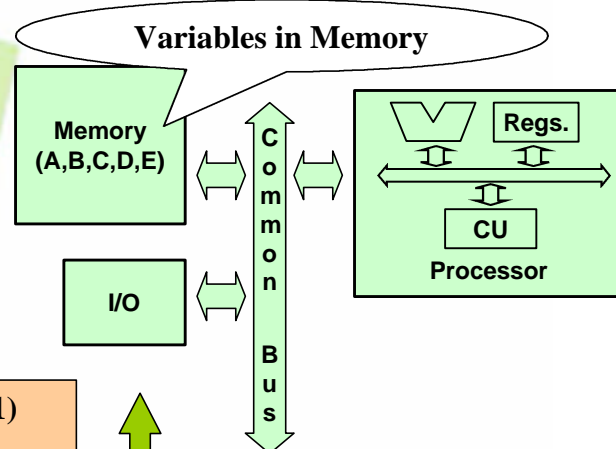

```
if (Sel==1)
  D=A;
else
  D=B;
E=D+C;
```



## It's VHDL

---

What is VHDL  
Abstraction Level  
HDL Design Flow

## What is VHDL ?

---

- **VHSIC Hardware Description Language**
  - | VHSIC : Very High Speed Integrated Circuits
- Originally Designed for Documentation
- A Simulation Language for Digital System
- Highly Structured, Strongly Typed(ADA-Like)
- A Multi-Purpose Language

## VHDL: Multi-Purpose Language

---

- Sequential Description
- Concurrent Description
- Netlist Language
- Timing Specification
- Self-Contained Test Language (“TestBenches”)



## VHDL : History

---

- First Generated in 1981 under VHSIC program
- Development Started in 1983
- Maintained by IEEE since 1987(IEEE1076-87)
- MIL-STD-454 Requires VHDL for All ASICs Delivered to DoD (1988)
- IEEE1164: Multi Valued Logic System, 1992
- Revised Standard “VHDL-93”
- VITAL Initiative Defines Standard Format for Gate Libraries,1994




## VHDL : Subgroups


- 8 Subgroups
- IEEE 1076 Subgroups
  - IEEE 1076.1 - Analog Standard
  - IEEE 1076.2 - Math Package
  - IEEE 1076.3 - Synthesis Package (std\_logic, arithmetic)
  - IEEE 1076.4 - VITAL
- Other EDA Industry WG/SG (<http://www.eda.org>)
  - SDF : Standard Delay Format (PAR1497)
  - VHDL-MW : Microwave Extension
  - WAVES : Waveform and Vector Exchange(STD1029.1-91)
  - OOVHDL, OMF, VHDL-MW, CODESIGN, ....



## Abstraction ( ) Level

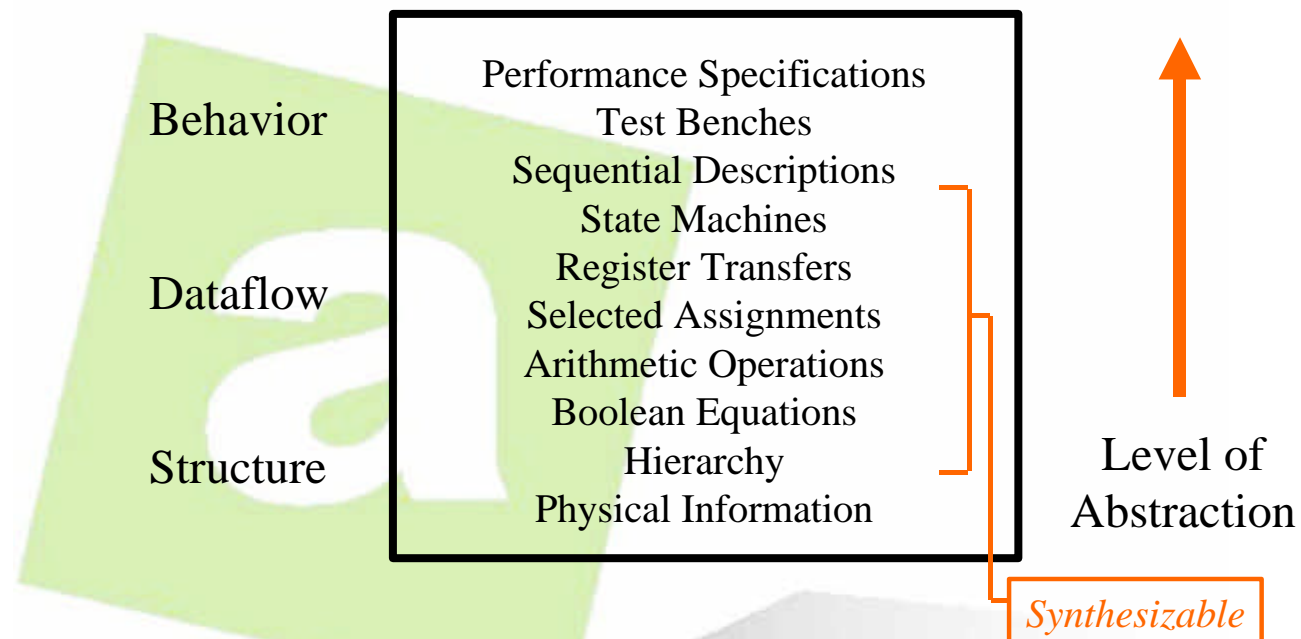

# Abstraction Level Comparison

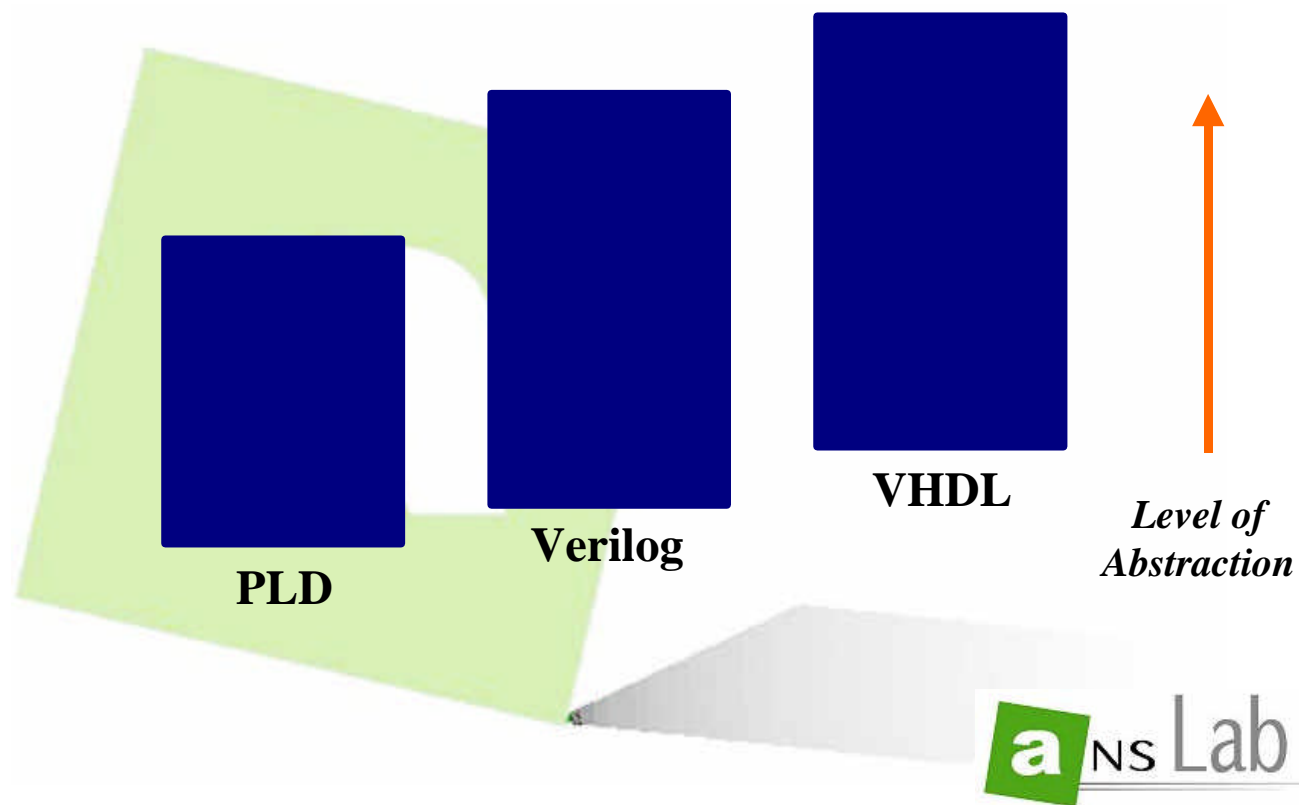

## Abstraction Level : Behavioral

- Sequential statements
- Implied registers (like a software programming language)
- Few (expensive) Synthesis tools available at this level
- Simulation, Modeling, and Specification

```
/* Programming Language */
```

```
int a, b, c;  
a = b;  
b = c;
```

```
-- VHDL  
-- testbench clock generator  
clock: process  
constant PERIOD := 100 ns;  
variable c: std_ulogic := '0';  
begin  
  wait for PERIOD / 2;  
  c := not c;  
  Clk <= c;  
end process;
```

```
-- VHDL  
-- Register inference  
clock: process(Clk)  
begin  
  if (Clk='1' AND Clk' EVENT) then  
    q <= d;  
  end if;  
end process;
```

**a**NS Lab

## Abstraction Level : Dataflow

---

- Concurrent assignments
- Explicit registers (like a PLD language)
  - User specify where registers are.
- Most Synthesis tools are at this level.

```
signal a,b,c,d,q;  
begin  
  c <= a and b;  
  b <= c and d;  
  q <= d when (clk=' 1' and clk' event);  
end;
```



## Abstraction Level : Structural


---

- Connected components (like a netlist)
- Extracted VITAL/Timing models after Place & Route

```
component nand2  
  port ( i0, i1 : std_logic; o : out std_logic);  
end component;  
signal a, b, c, d;  
begin  
  u1 : nand2 port map (i0 => a, i1 => b, o => c);  
  u2 : nand2 port map (i0 => c, i1 => d, o => a);  
end;
```



## HDL Design Flow

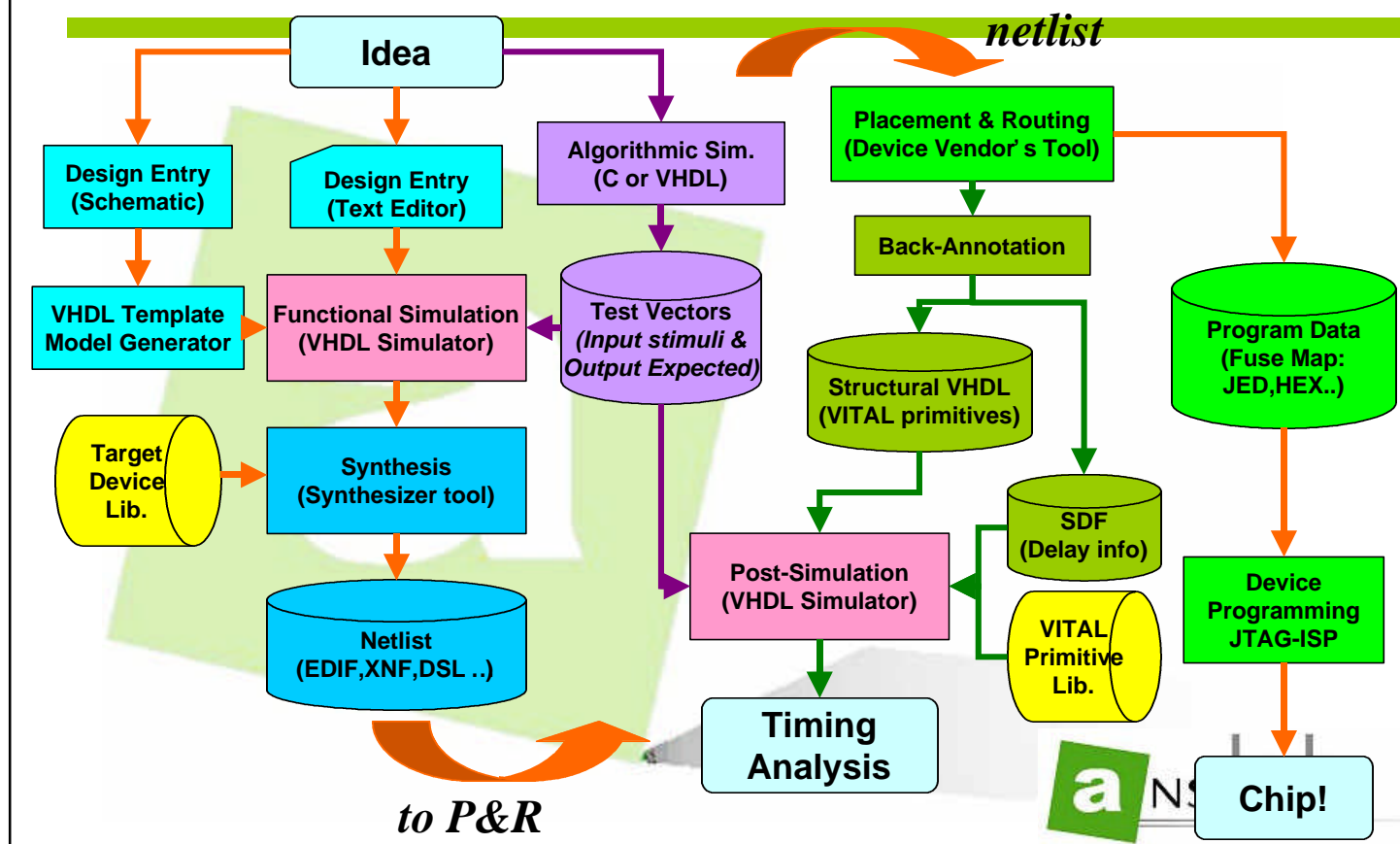


## Design Entry (HDL)


- Text Editor
- Language Sensitive Text Editor
  - Keyword coloring
  - Statement Template
- Visual Entry Tools
  - Template & Translate (Structural)
- Testbench
  - Converter (Waveformer)



# HDL Design Entry (Text Editor)

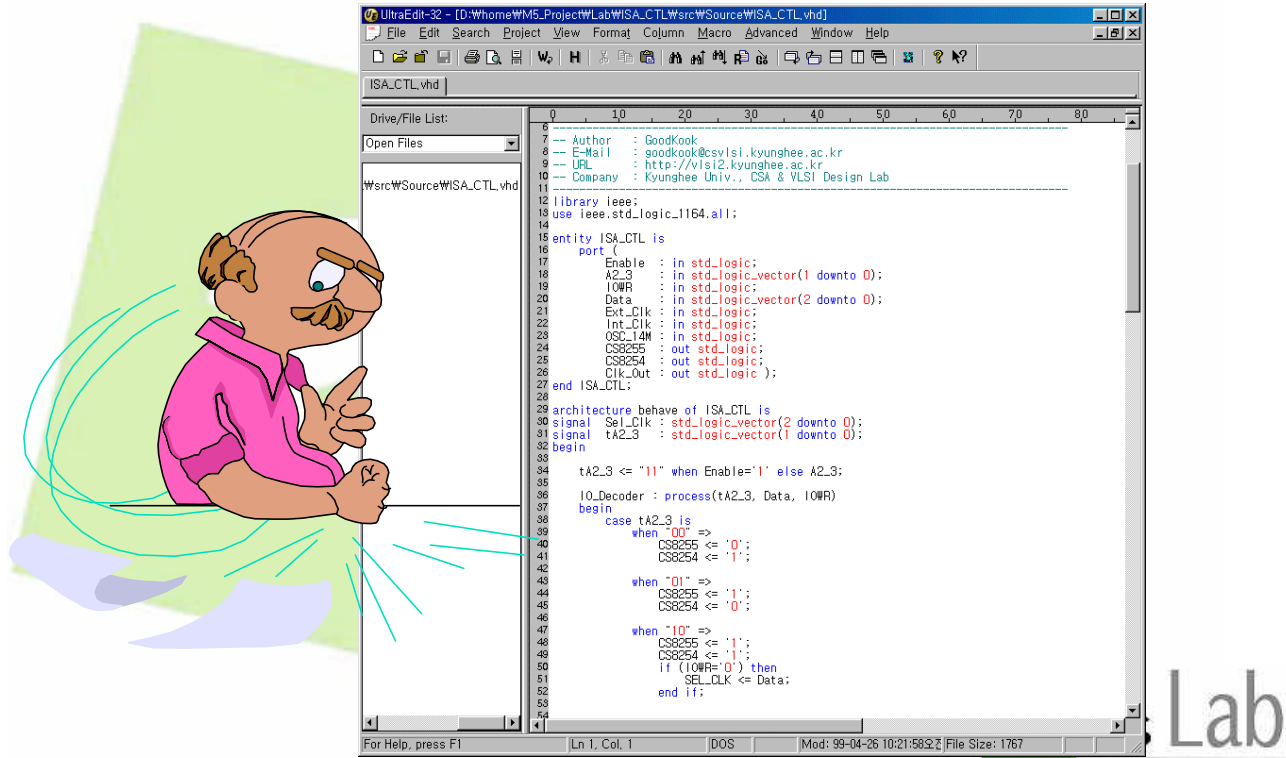

# HDL & Schematic Mixed

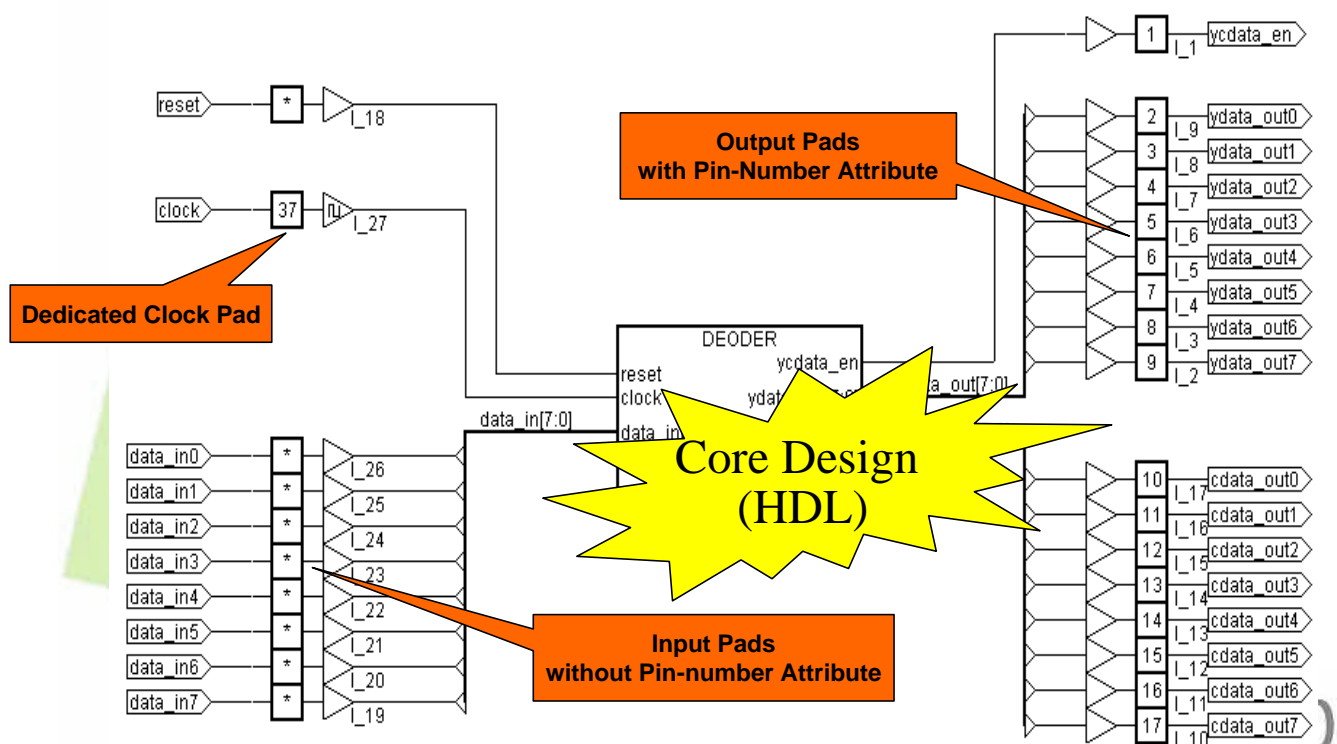

# HDL Design Entry (Visual Tools)

- Mentor's Renoir
- Aldec's ActiveHDL
- StateCAD
- Synario
- Summit VisualHDL

**Visual Entry**

- FSM
- Block Diagram
- Truth Table
- Flow Chart
- Schematics

**HDL Source**  
(VHDL, Verilog)




# HDL Simulation

```

entity ISA_CTL is
port (
  IOWR : in std_logic;
  CS8254 : out std_logic;
  Clk_Out : out std_logic;
end ISA_CTL;
architecture behave of ISA_CTL is
  signal Sel_Clk : std_logic_vector(2 downto 0);
begin
  IO_Decoder : process(tA2_3, Data, IOWR)
  begin
    case tA2_3 is
      when "00" =>
        CS8255 <= '0';
        CS8254 <= '1';
      when "10" =>
        if (IOWR='0') then
          SEL_CLK <= Data;
        end if;
        ....
      end case;
    end process;
  end behave;
end
    
```

**VHDL Source**

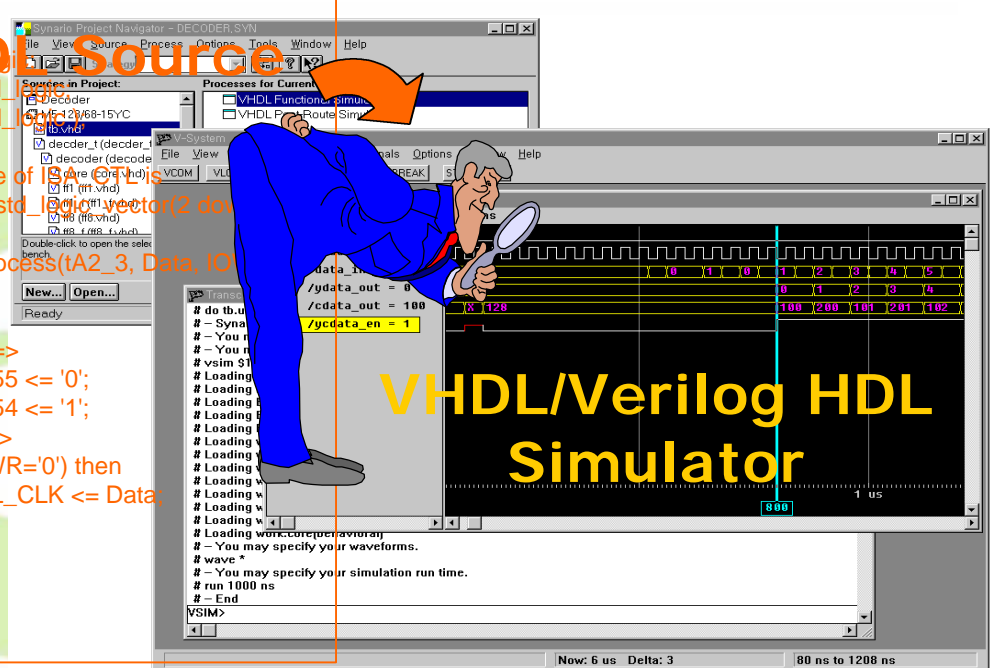

# HDL Synthesis

HDL Hardware (Netlist)

Logic Optimization

```

entity ISA_CTL is
port (
    IOWR : in std_logic;
    CS8254 : out std_logic;
    CLK_Out : out std_logic );
end ISA_CTL;
architecture behave of ISA_CTL is
    signal Sel_Clk : std_logic_vector(2 downto 0);
begin
    IO_Decoder : process(tA2_3, Data, IOWR)
    begin
        case tA2_3 is
            when "00" =>
                CS8255 <= '0';
                CS8254 <= '1';
            when "10" =>
                if (IOWR='0') then
                    SEL_CLK <= Data;
                end if;
            .....
        end case;
    end process;
end behave;
    
```

VHDL Source

EDIF Netlist

```

(edif isa_ctl
(edifVersion 2 0 0)
(edifLevel 0)
(keywordMap (keywordLevel 0))
(status
(written
(timestamp 1999 06 01 00 15 49)
(program "Leonardo Spectrum Level 3"
(version "v1998.2e")
(author "Exemplar Logic Inc")))
(external PRIMITIVES
(edifLevel 0)
(technology (number/Definition ))
(external mnc
(edifLevel 0)
(technology (number/Definition ))
(cell OR3 (cellType GENERIC)
(view NETLIST (viewType NETLIST)
    
```

# Device Implementation

Place & Route/ASIC Chip


Full/Semi-Custom Design(STD Cell/Gate Array)

PLD(CPLD/FPGA)

Vendor P&R Tool

ASIC Foundry (SEC, Hyundai, ...)

My Custom Chip NOW

 

## About PLD


---

Programmable Logic Device
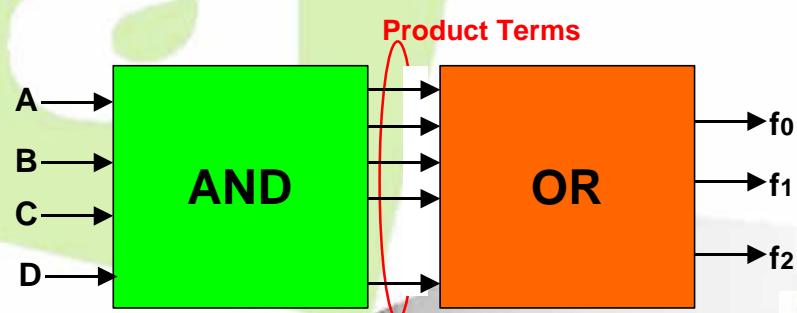
## PLD : “Sum of Products”

---

- Programmable Logic Device
- Combinational Logic Circuits
  - “Sum of Products”
    - AND Plane (product term)
    - OR Plane (sum)



# PLD : ROM and PLA

## Combinational Logic Circuit

### ROM Device


- | AND Plane Fixed (Address Decoder)
- | OR Plane Programmable

### PLA (Programmable Logic Array)


- | AND Plane Programmable
- | OR Plane Programmable



# PLD : PLA Internal

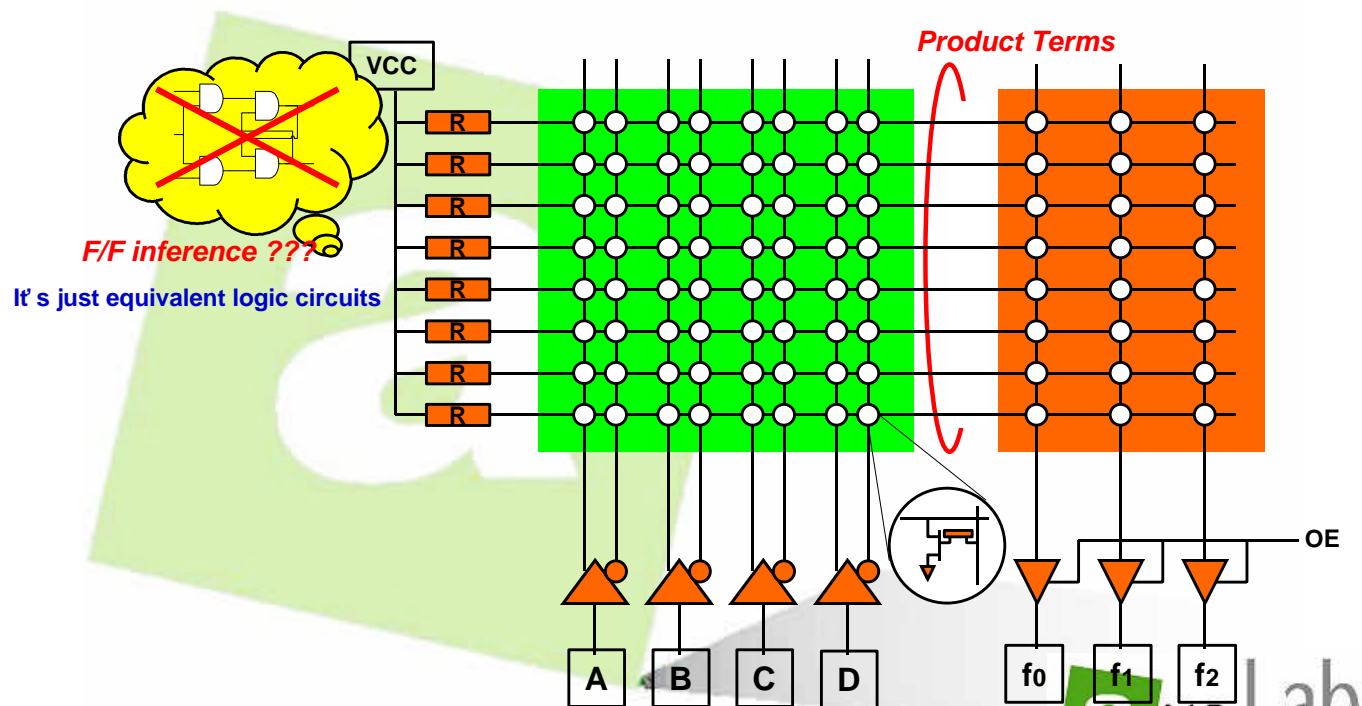


## PLD : PLA with output F/F

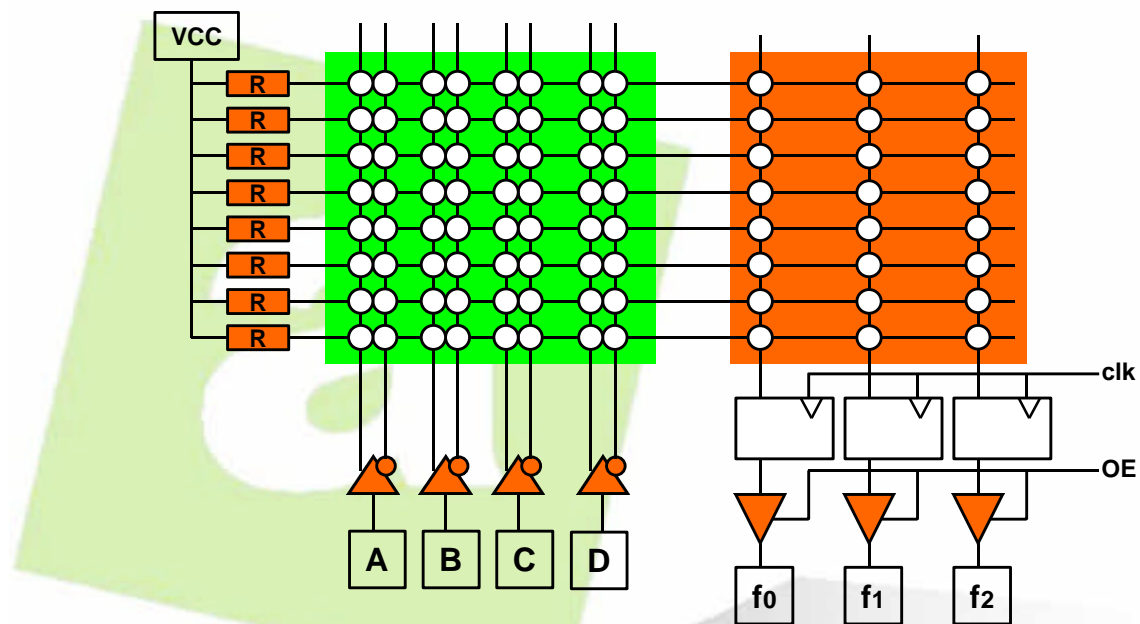


**a**NS Lab

## PLD : Complex PLD

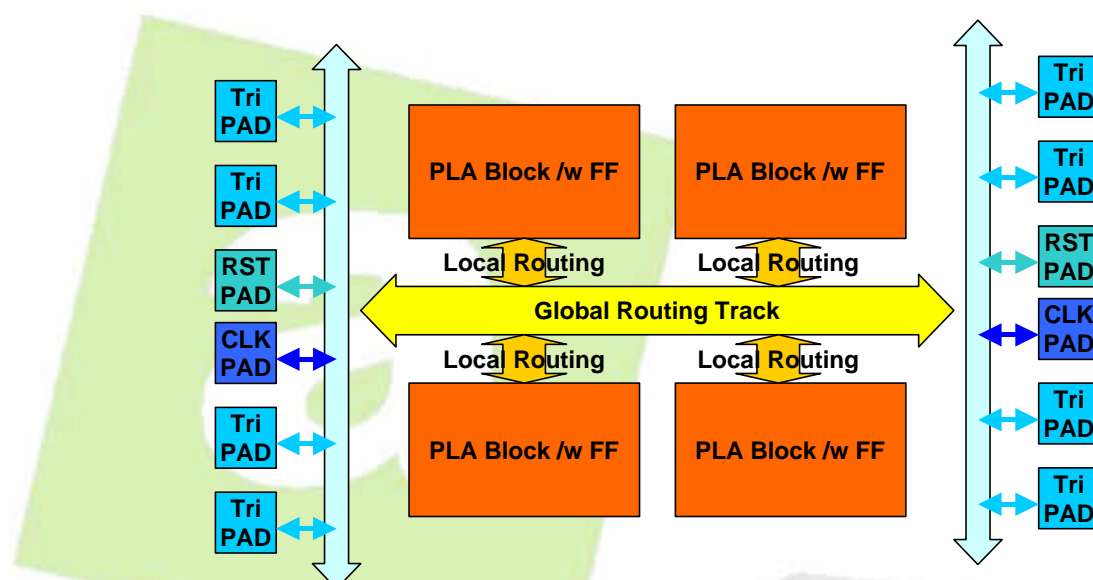


**a**NS Lab


## PLD : FPGA Internal

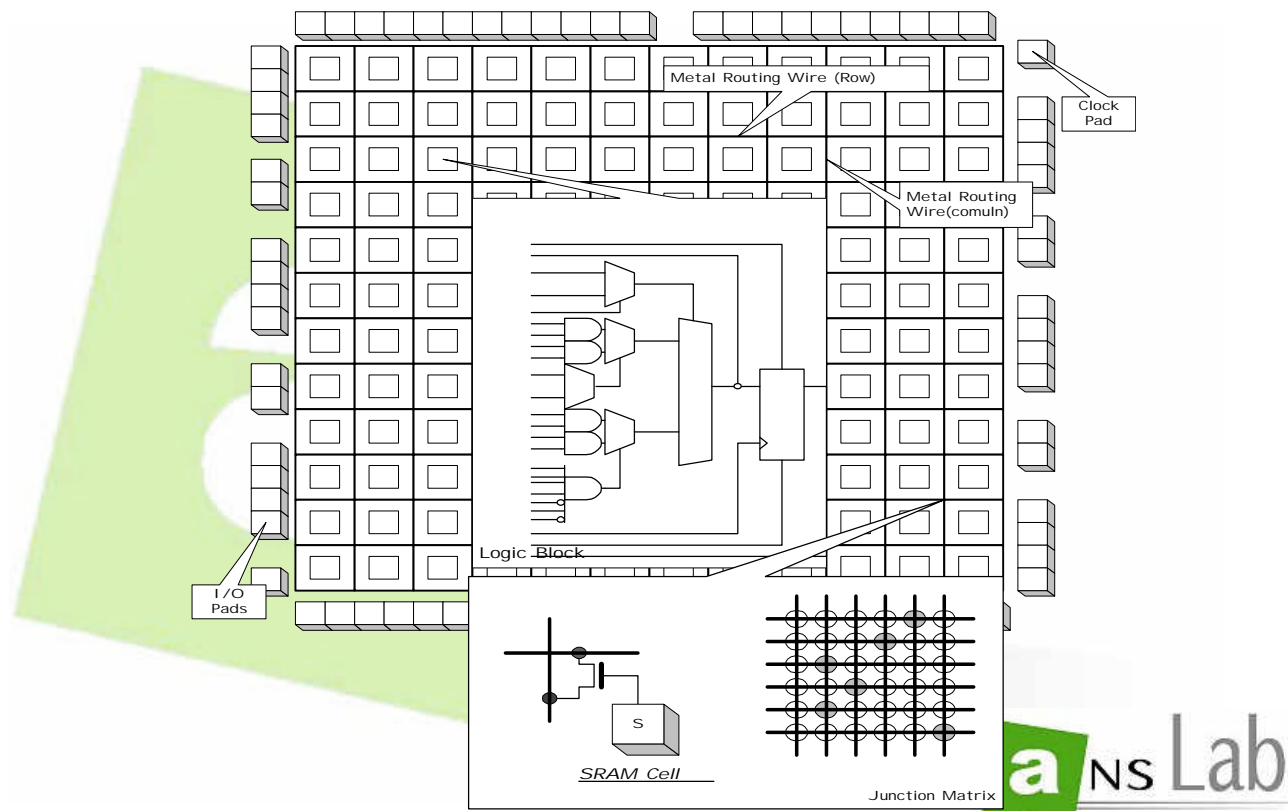

## PLD : Interconnect (Junction Photo)

 


## PLD : Logic Cell (QuickLogic)

 

**a**NS Lab


## PLD : Logic Cell (cont' ed)

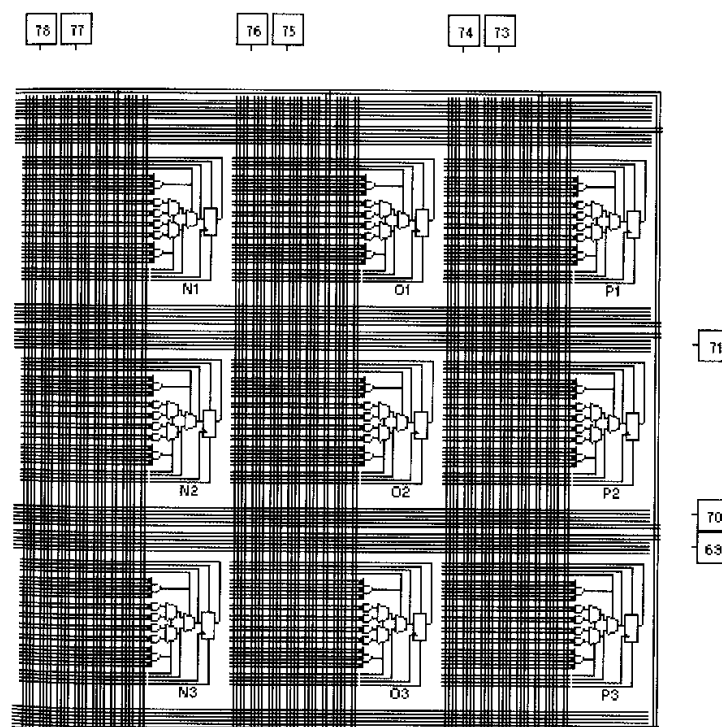

**a**NS Lab



# PLD : CPLD (Mach5 Internal)

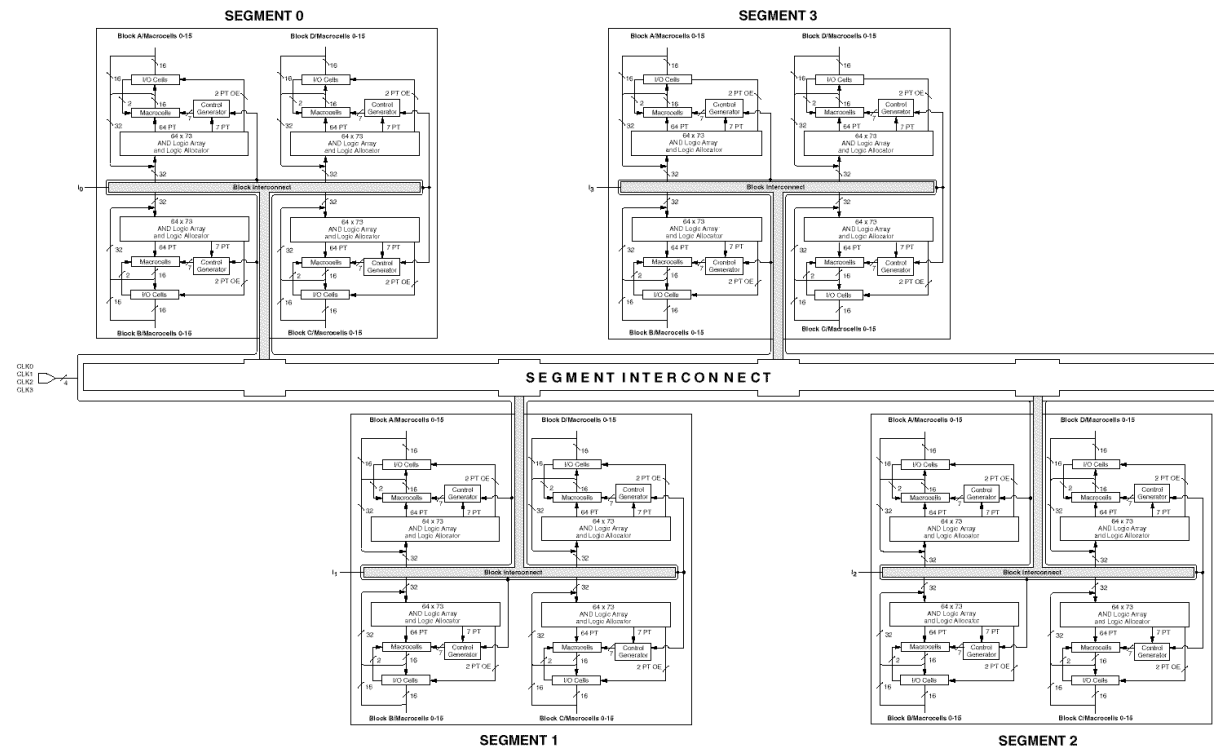

# PLD : CPLD (Mach5 PLA Block)


 


Figure 8. M5-256 PAL Block


# PLD : Flex10k Internal Block

Figure 1. FLEX 10K Device Block Diagram

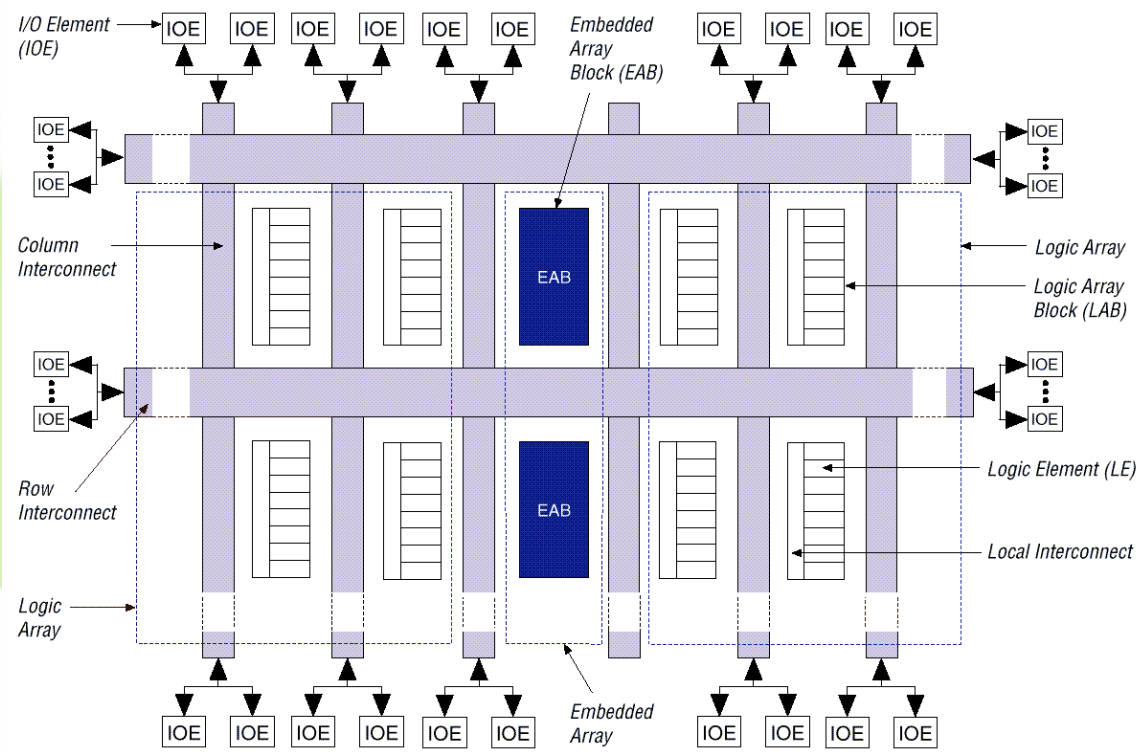


# PLD : Flex 10k EAB

Figure 4. FLEX 10K Embedded Array Block

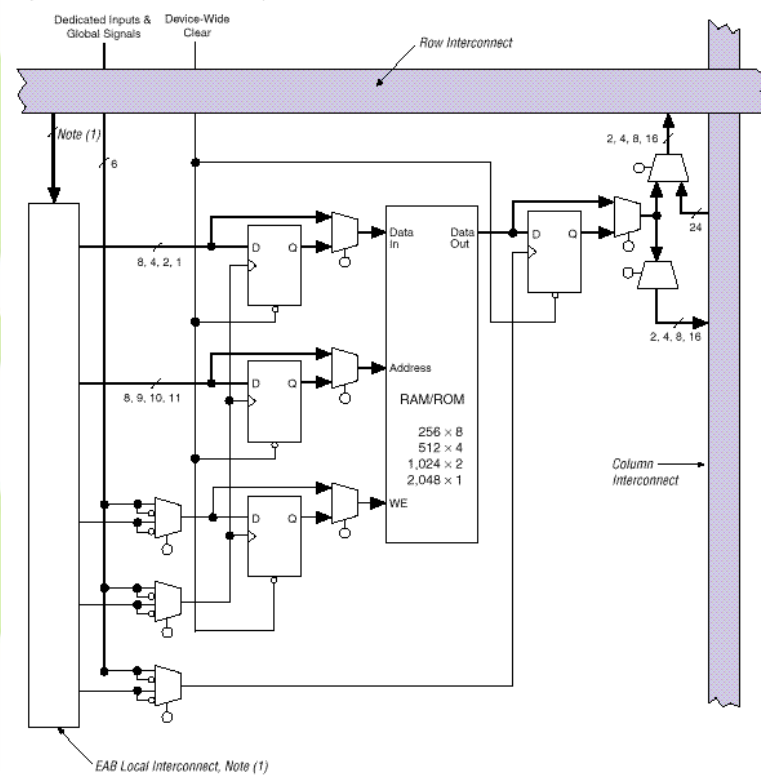

# PLD : Flex 10k LAB

Figure 5. FLEX 10K LAB

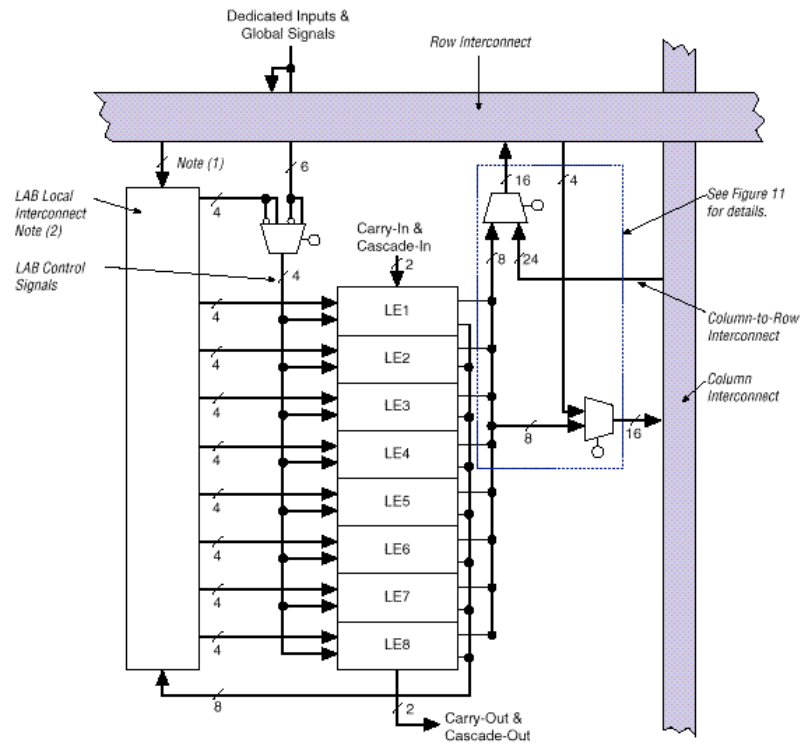

# PLD : Programming

- ROM
  - Standard Programming Method
  - Generalized Writing Device
    - PROM
    - UV-EPROM
    - EEPROM
- CPLD/FPGA
  - No Standard internal structure
  - Vendor's Writing Device
    - UV-ROM Type
    - PROM Type (OTP, Anti-Fuse)
  - ISP & JTAG
    - EEPROM Type (ISP)
    - SRAM Type




# PLD : Programming - ISP

## In-System Programmability

- Time-to-Market
- Low price
- PCB testing capabilities

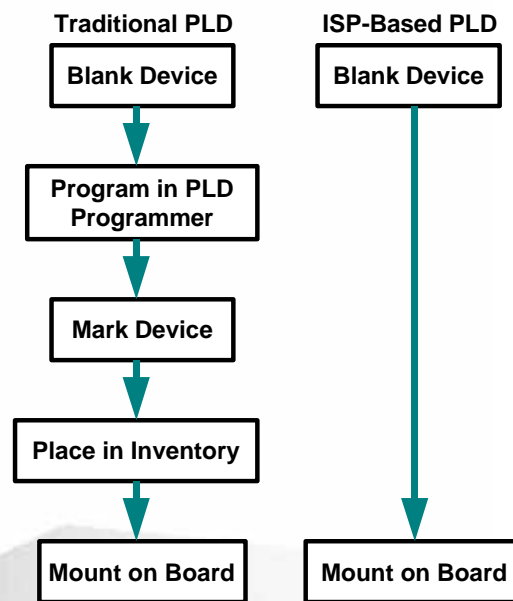
## JTAG

- Joint Test Action Group
- Standard IEEE 1149.1-1990
- PLD Program/Test
- Verify PCB & PLD Internal
- Simplified system test




# ISP Benefits

## Mount Unprogrammed

 


- Eliminates handling of devices
- Prevents bent leads

## Program In-System

 

- Allows generic end-product inventory
- Specific test protocol or algorithm can be programmed during prototyping, manufacturing or test flow

## Reprogram in the Field

 


- No need to return system for upgrades
- Add enhancements quickly & easily






# Boundary Scan Architecture

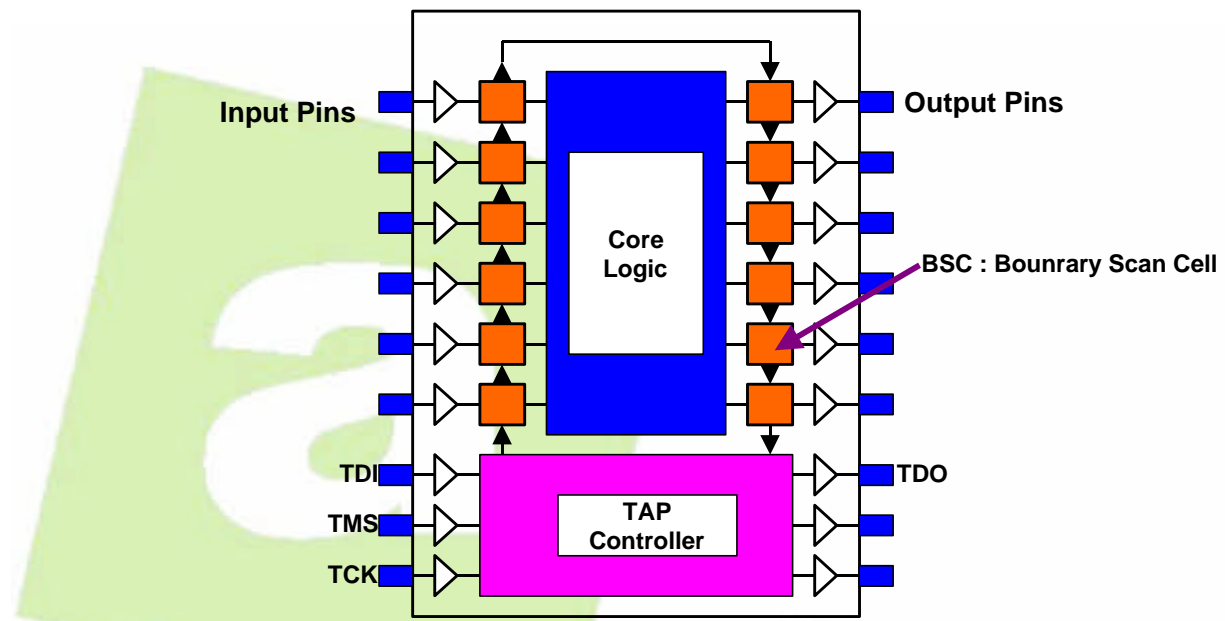

Test Access Port Controller controls Boundary Scan-Path



# JTAG Connectivity Test Example

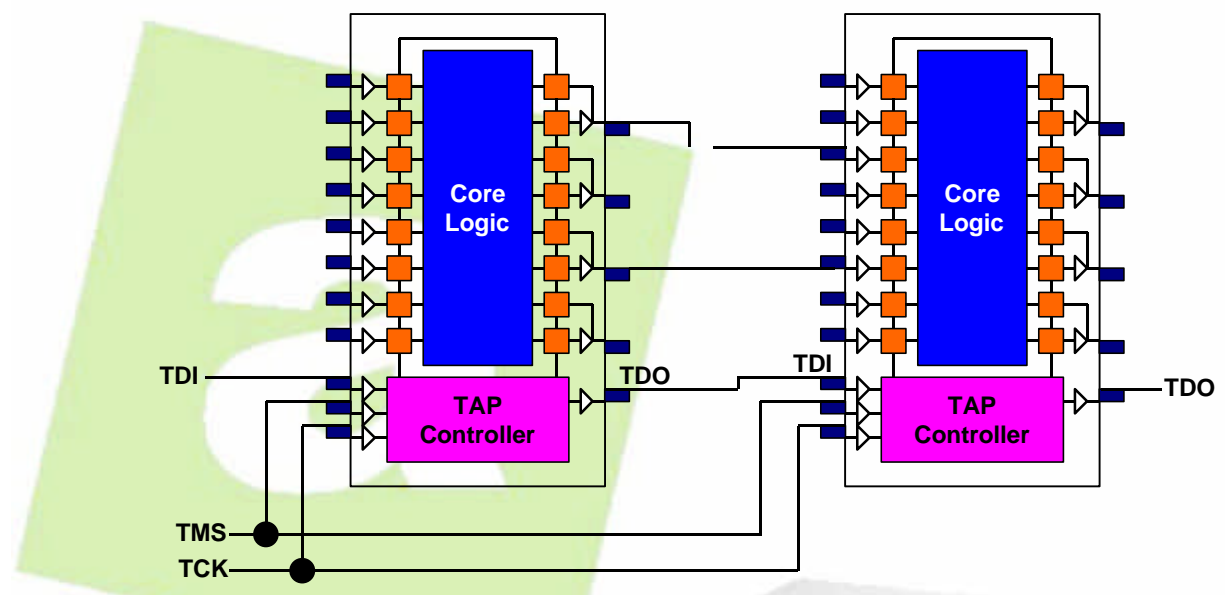

# TAP Controller

---

- A State Machine to control TAP
  - TAP : TDI,TDO,TMS,TCK,/TRST
- Control Operations
  - Shifting Test Data
  - Sampling Data
  - Driving a value
- Can pause while shifting registers
- Controls input BSC and output BSC separately



# VHDL

---

# VHDL

...

- Programming Language Compiler
  - Algorithm Test
  - Test Vector Generation
- HDL Simulator
  - Functional Simulation
  - Timing Simulation
- HDL Synthesizer
  - HDL to Netlist
  - Optimization
- Device Vendor Tool (Design Kit)
  - Place and Route
  - Timing Extraction

**a**NS Lab

## VHDL Simulator (PC Version)

- ModelSim (Ex. V-System)
  - <http://www.model.com>
  - Support VHDL/Verilog, FLI/PLI
- Aldec ActiveVHDL
  - <http://www.aldec.com>
  - Visual tool included(FSM, Block editor)
- PeakVHDL
  - <http://www.acc-eda.com>
- VeriBest
  - <http://www.veribest.com>
- MyVHDL ( )
  - <http://www.seodu.co.kr>

**a**NS Lab



## VHDL Synthesizer (General PLD)


- Metamor Logic Synthesizer
- MINC PLSynthesizer
- Synopsys' FPGA Express/FPGA Compiler
- Synplicity' s Synplify
- Exemplar Galileo/Leonardo/Spectrum

■ :

■ <http://www.optimagic.com>




## VHDL Designer

 


# VHDL: Design Unit

## Entity and Architecture

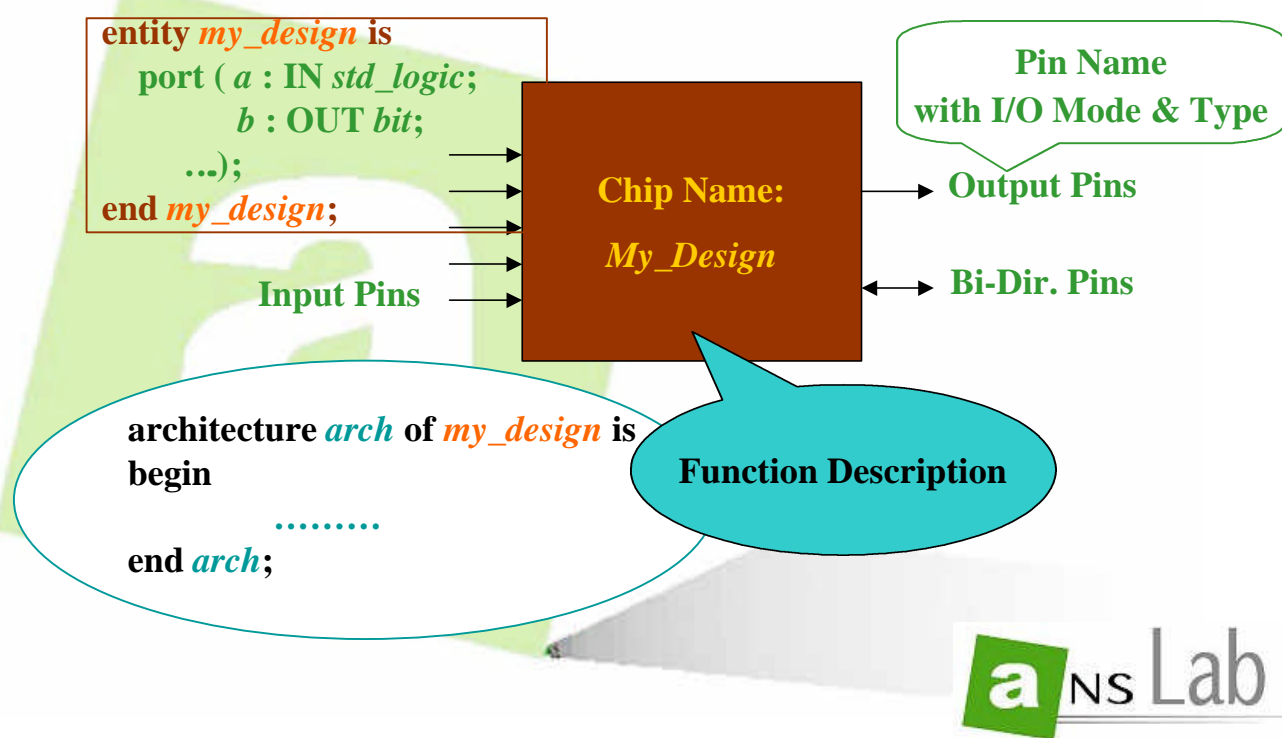

# VHDL : Configuration

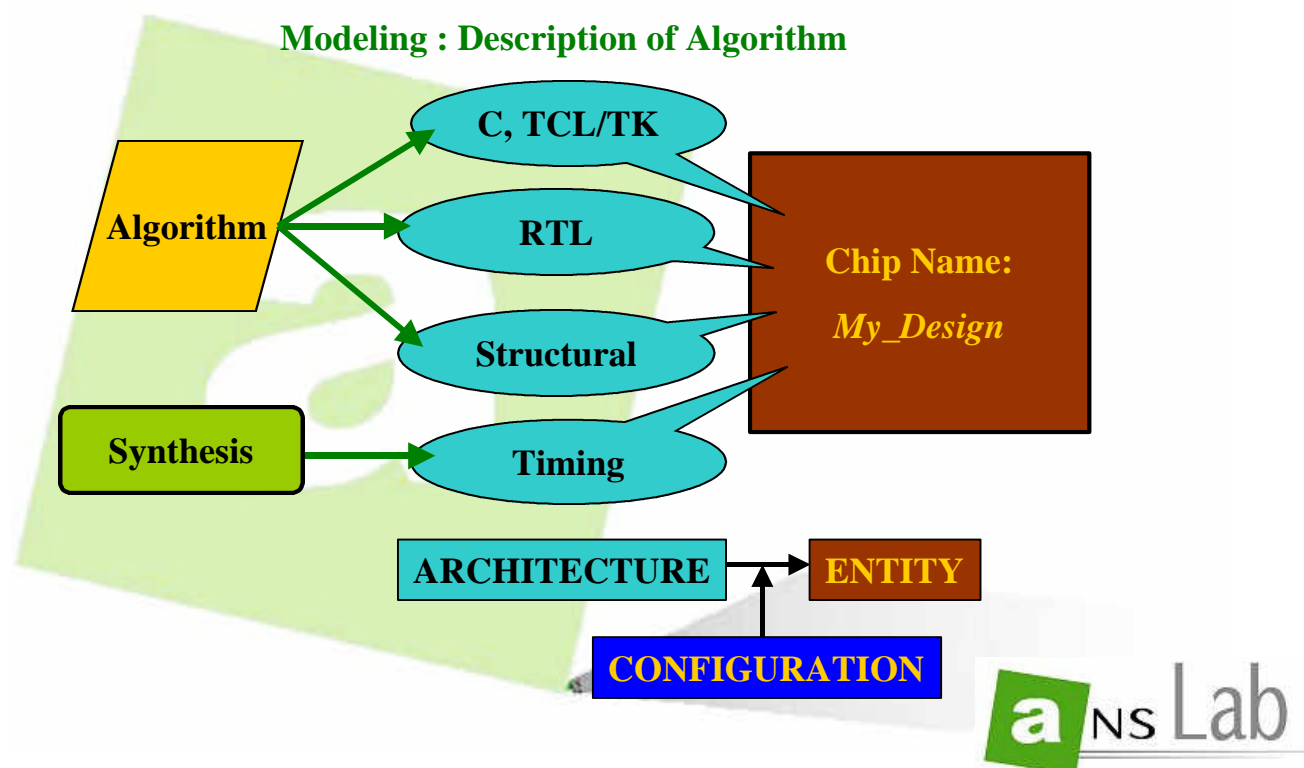

## VHDL Testbench

---

## VHDL Testbench

---

- **NO Synthesis VHDL**
- **Large/Complex Test Vectors and Verify Automated**
  - “Think DSP Application or MPU’s Complex IO”*
- **Test Vectors**
  - **Input Vector**
  - **Output Vector**
  - **Expected Vector**
- **UUT : Unit Under Test**
- **Clock Generator**
- **Error Report Utility**

## Library : STD


### Library for Testbench

```
use std.standard.all; -- Char. & String type define  
use std.textio.all; -- Text IO Buffer & File IO
```


### Testbench Entity

```
ENTITY test_prep1 IS  
    -- Testbench has NOT need Port ....  
END test_prep1;
```

## Testbench Component

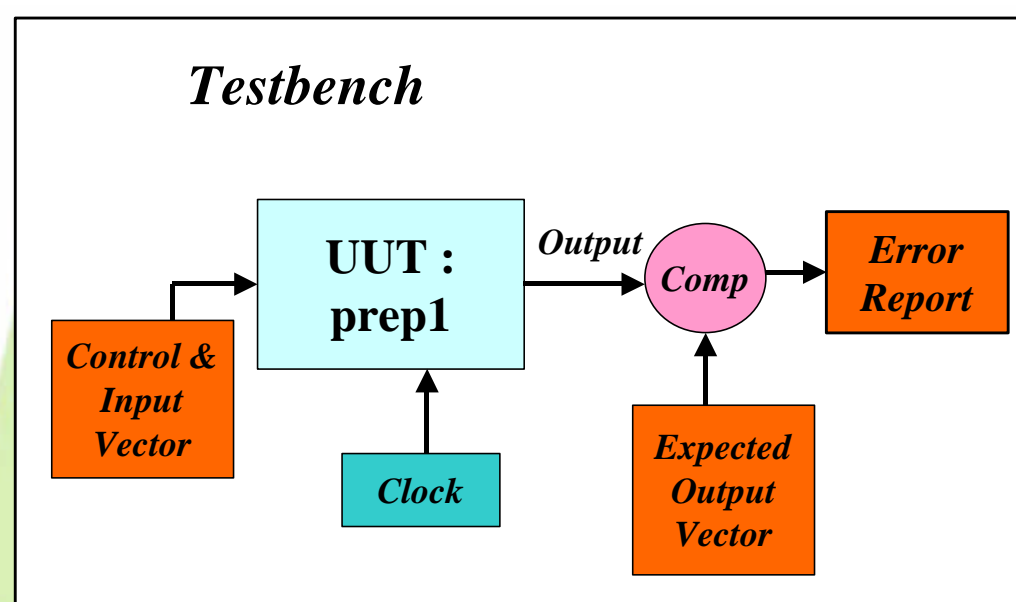

## Testbench (Test Vector : File I/O)

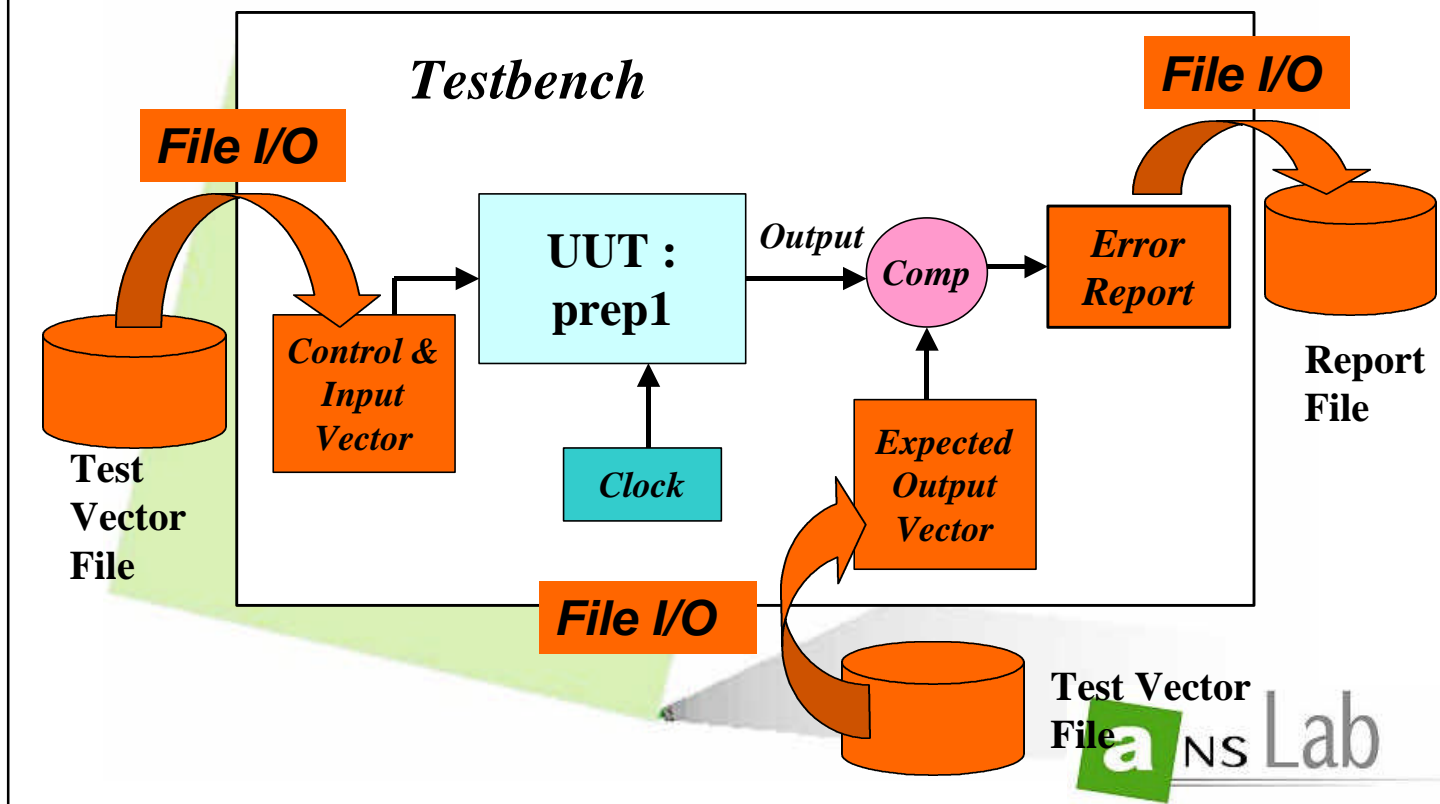


## Advanced VHDL Environment

H/W & S/W Co-Simulation  
Scripting (Macros, Tcl/Tk)  
Visual Tools

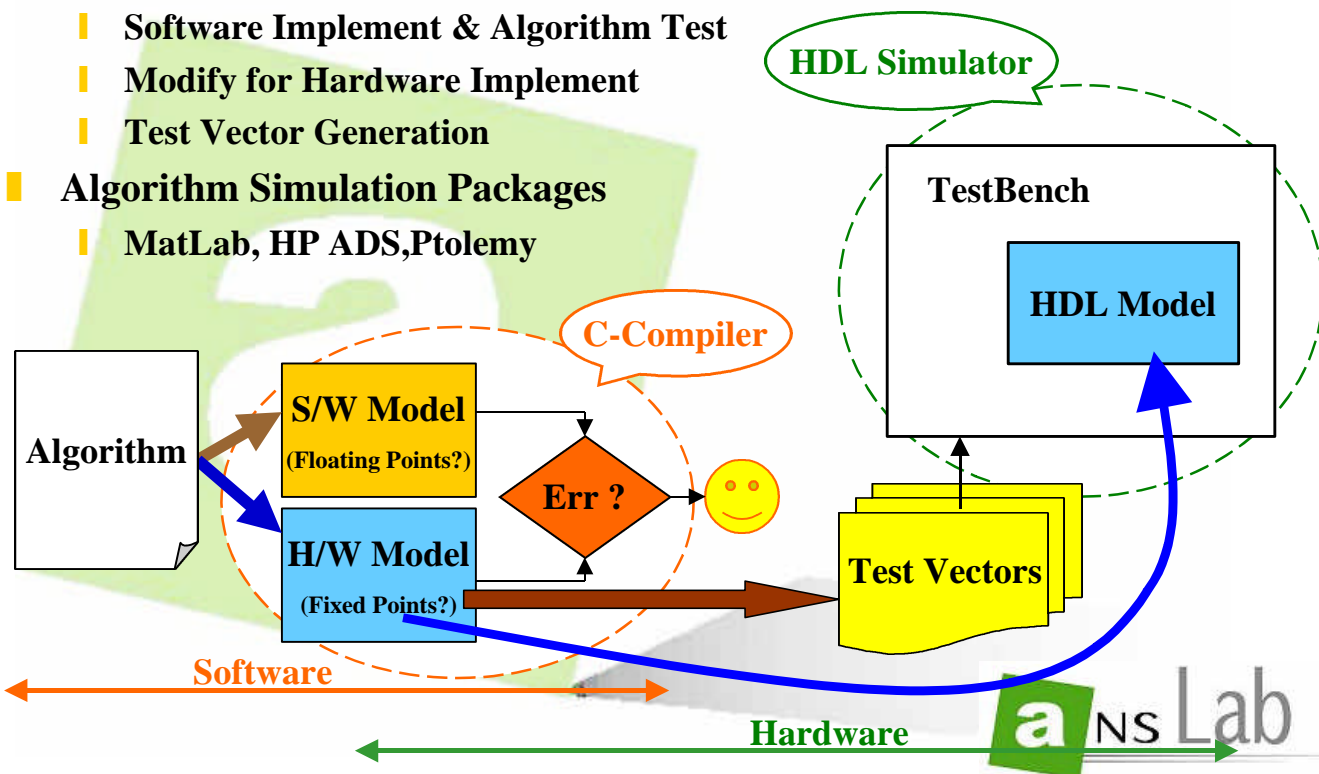
# S/W & H/W Modeling/Simulation

- Programming Language Model
  - Software Implement & Algorithm Test
  - Modify for Hardware Implement
  - Test Vector Generation
- Algorithm Simulation Packages
  - MatLab, HP ADS, Ptolemy


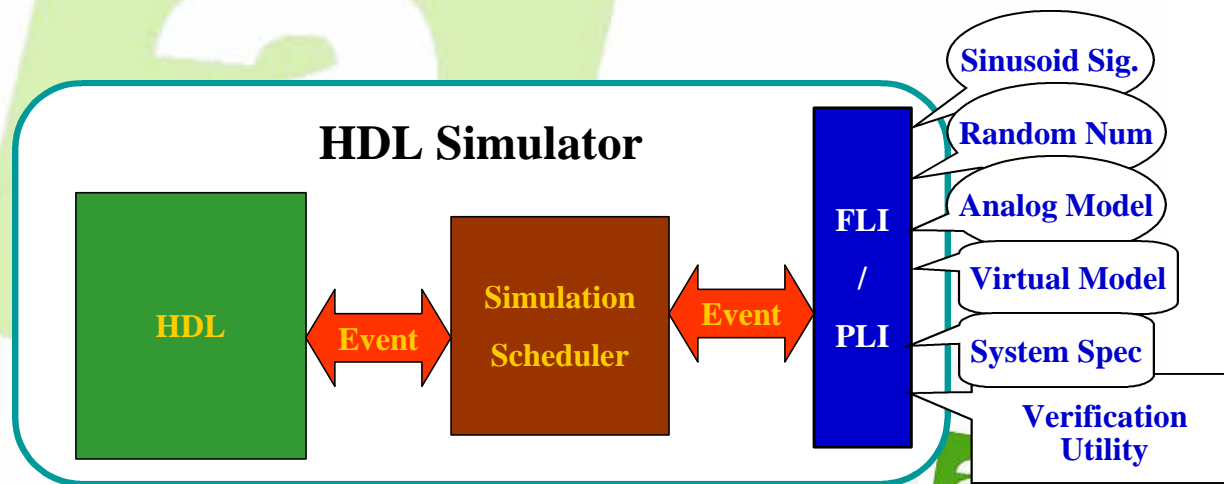
# H/W & S/W Co-Simulation

- Software Model for Test & Verification
  - Easy & Fast : Specification/Documentation/Test
  - Complicated test signal generation
  - Direct verification at modeling process
  - Expecting synthesis result
- Co-Simulation How ?
  - Use Shared Library Executables (.dll, .so)
  - Call-Back to signal event by HDL Simulator (Scheduling)
  - Interface to H/W Signal Types



## Using Scripts

- Need for Reusability of IP
- Macro Files
  - Simulation Commands
- Tcl/Tk
  - GUI : Visualize Simulation Result
  - Integration of External EDA Tools/Utilities
  - Build Design Specific User Interface



## Visual Tools

- Visual Tool
  - Graphical Design Entry & HDL Generation
  - Easy & Familiar
  - View whole design : Interconnection between IP Blocks, Good for System integration
- What Tools avail ?
  - Keyword Colored Text Editor, Context Sensitive Help
  - Schematics
  - Block Diagram Editor
  - Truth Table Entry
  - Finite-State Machine
  - Flow Chart
  - TestBench Generation, Language Template, etc.,...



## VHDL Data Types

---

Scalar Types  
Composite Types

## Data Types (VHDL )

---

- All signals have a type
- Type checking is strict !
- Each type has a defined set of valid operations
- Each type has a defined set of values
- Types are user-extendable



# VHDL Data Types ( )

---

- Scalar Types
  - Enumeration Type
  - Integer Type
  - Floating-Point Types
  - Physical Types
- Composite Types
  - Array Types
  - Record Types
- Access Types
- File Types



# Common Types

---

- Bit (or `std_logic`, defined by IEEE 1164)
- Bit\_vector (or `std_logic_vector`)
- Boolean
- Integer
- Character
- String
- Enumerated type



## More Types

- Real (floating point)
- Physical (time, current, etc.)
- Arrays (single- and multi-dimensional, constrained or unconstrained)
- Records
- Access types (pointers)
- File types



## Enumerated Types

- Many common VHDL types are actually enumerated types:
  - Boolean (TRUE, FALSE);
  - Bit (1,0)
  - char
- User extendable:

```
type Boolean is ( FALSE, TRUE);  
type bit is ('0', '1');  
type std_ulogic is ('U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-');  
type states is ( IDLE, RECEIVE, SEND);
```



## Enumerated Type Encoding

- One Hot Encoding (State Machine)
- Binary Encoding

	bit2	bit1	bit0
IDLE	-	-	1
RECEIVE	-	1	-
SEND	1	-	-

**OneHot**

	bit1	bit0
IDLE	0	0
RECEIVE	0	1
SEND	1	0

**Binary**



## Integer and Real Type

- Integer Type (Synthesizable)

```
type integer is range -2147483647 to 2147483647; -- VHDL Predefined
-- 32-bit signed integer

type my_integer is range 0 to 15; -- 4-bits
signal count : my_integer;
signal count : integer range 0 to 15; -- count(0) : LSB, count(3) : MSB
```

- Floating-Point Type (NOT Synthesizable)

```
type real is range -1.0E38 to 1.0E38; -- VHDL Predefined
type my_real is range 0.0 to 1.0; -- VHDL Predefined
```



## Physical types

- Represent relations between quantities
  - NOT Synthesizable
- Example : “time”

```
type time is range -2147483647 to 2147483647
units
  fs;
  ps = 1000 fs;
  ns = 1000 ps;
  us = 1000 ns;
  ms = 1000 us;
  sec = 1000 ms;
  min = 60 sec;
  hr = 60 min;
end units;
```



## Array Types

- Synthesizable
- Array Example (Unconstraint)

```
type std_ulogic_vector is array ( NATURAL RANGE <> ) OF std_ulogic;
type UNSIGNED is array (NATURAL range <> ) of BIT;
type SIGNED is array (NATURAL range <> ) of BIT;
type matrix is array (natural range <>, natural range <>) of bit;
```

- Array Example (Constraint)

```
type byte is array (7 downto 0) of bit;
```



# Record Type

## ■ Example

```
type month_name is (jan,feb,mar,apr,may,jun,jul,aug,sep,oct,nov,dev);
type date is
record
  day : integer range 1 to 31;
  month : month_name;
  year : integer range 0 to 4000;
end record;
```

```
constant my_birthday : date := (21, nov, 1963);
```

```
SIGNAL my_birthday : date;
```

```
my_birthday.year <= 1963;
my_birthday.month <= nov;
my_birthday.day <= 21; -- 5-bit
                        -- my_birthday(0) : LSB
                        -- my_birthday(4) : MSB
```

 ANS Lab

# Subtypes and Type Conversion

## ■ Type checking is strict !

## ■ Type with constraint

```
subtype <subtype_name> is <base_type> [<constraint>];
```

## ■ Type Conversions

```
<type>(<expressions>)
```

 ANS Lab

## VHDL type checking is strict !

```
type big_integer is range 0 to 1000;
type small_integer is range 0 to 7;

signal intermediate : small_integer;
signal final : big_integer;

final <= intermediate * 5; -- type mismatch error
```

or

```
type big_integer is range 0 to 1000;
subtype small_integer is big_integer range 0 to 7;

signal intermediate : small_integer;
signal final : big_integer;

final <= intermediate * 5; -- Same Base type
```

```
type big_integer is range 0 to 1000;
type small_integer is big_integer range 0 to 7;

signal intermediate : small_integer;
signal final : big_integer;

final <= big_integer(intermediate * 5); -- Type Conversion
```



## IEEE 1076 Predefined Types

```
type bit is ('0', '1');
type bit_vector is array (integer range <>) of bit;
type integer is range MININT to MAXINT;
subtype positive is integer range 1 to MAXINT;
subtype natural is integer range 0 to MAXINT;
type boolean is (TRUE, FALSE);
```



## IEEE 1164 Predefined Types

- `std_logic`, `std_logic_vector` (resolved)
- `std_ulogic`, `std_ulogic_vector` (unresolved)
- Nine valued enumerated type
- Used as replacements for `bit`, `bit_vector`
- Used as the standard data types for system interfaces



## IEEE 1164 Predefined Types

```
TYPE std_ulogic IS ('U', -- Uninitialized
                   'X', -- Forcing Unknown
                   '0', -- Forcing 0
                   '1', -- Forcing 1
                   'Z', -- High Impedance
                   'W', -- Weak Unknown
                   'L', -- Weak 0
                   'H', -- Weak 1
                   '-' -- Don't care
                   );
type std_ulogic_vector is array (natural range <>) of std_ulogic;
subtype std_logic is resolution_func std_ulogic;
type std_logic_vector is (natural range <>) of std_logic;
subtype X01Z is resolution_func std_ulogic range 'X' to 'Z';
```



# Type Conversion Example

```
package my_type is
  type big_integer is range 0 to 1023;
  subtype small_integer is big_integer range 0 to 7;
end package;

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use work.my_type.all;

entity subtype_test is
  port ( a : in small_integer;
         b : in small_integer;
         c : out std_logic_vector(9 downto 0) );
end subtype_test;
architecture behave of subtype_test is
  signal t_int : big_integer;
begin
  t_int <= a + b; -- for subtype, type casting not needed !
  c <= std_logic_vector(to_unsigned(natural(t_int), 10)); -- type casting/type conversion
end;
```




# Type Conversion/Type Casting

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

type big_integer is range 0 to 1023; -- 10-bits
signal t_int : big_integer;
signal c : out std_logic_vector(9 downto 0);
```
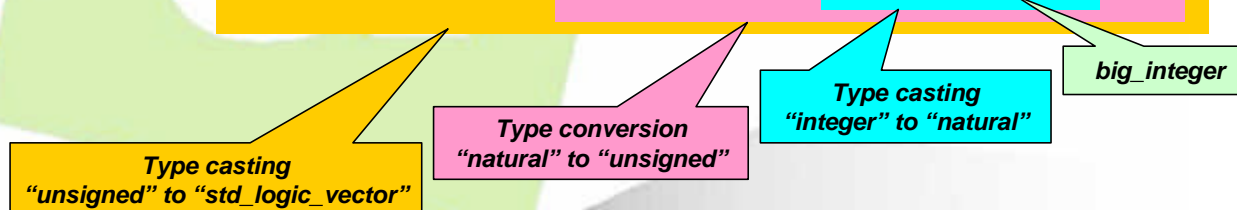
```
c <= std_logic_vector(to_unsigned(natural(t_int), 10));
```





## VHDL Design Partition

---

Processes  
Blocks  
Functions  
Procedures

## Processes and Blocks

---


### ■ Process

- Sequential Env.
- Local VARIABLE
- NOT Nested Process
- Sensitivity list or WAIT statement
- communicate with SIGNAL


### ■ Block

- Concurrent Env.
- Local SIGNAL
- Nested Blocks
- GUARDED expression

# Concurrent vs. Sequential

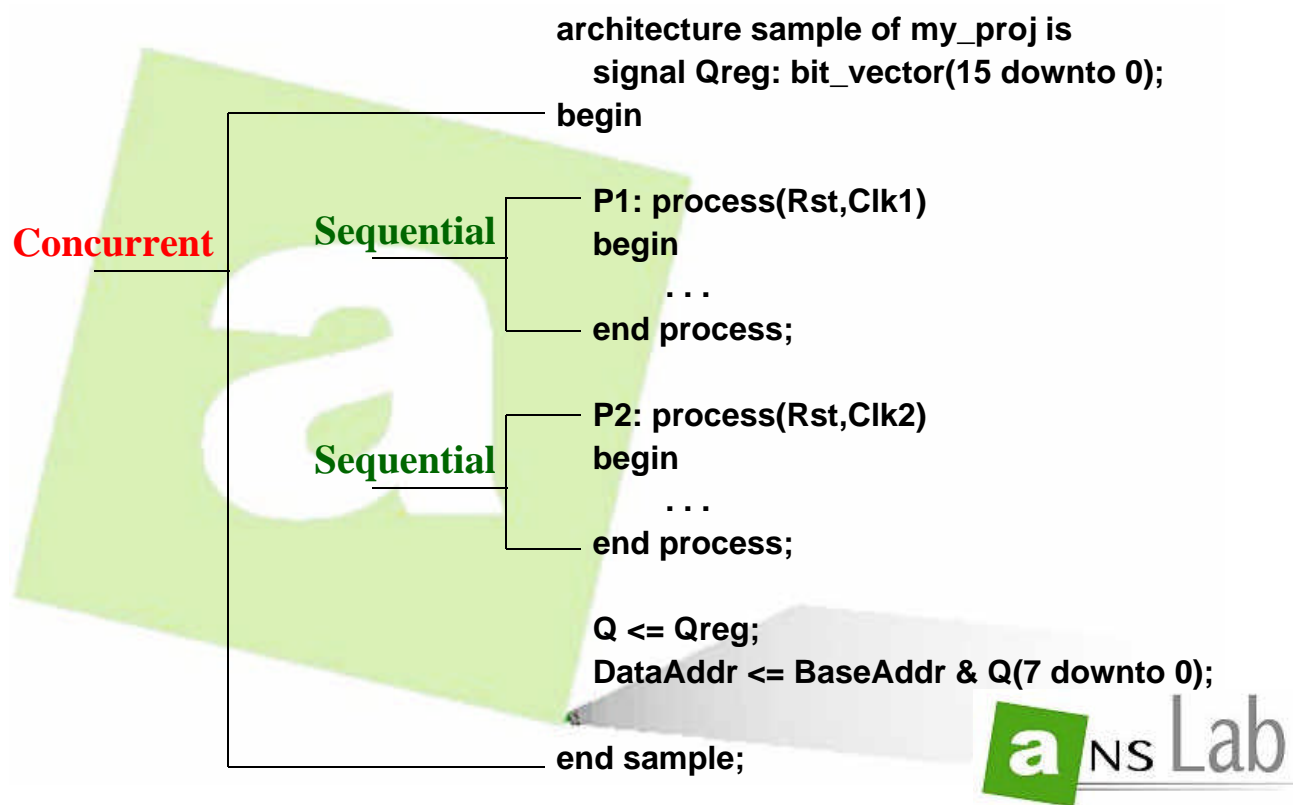

# Concurrent vs. Sequential

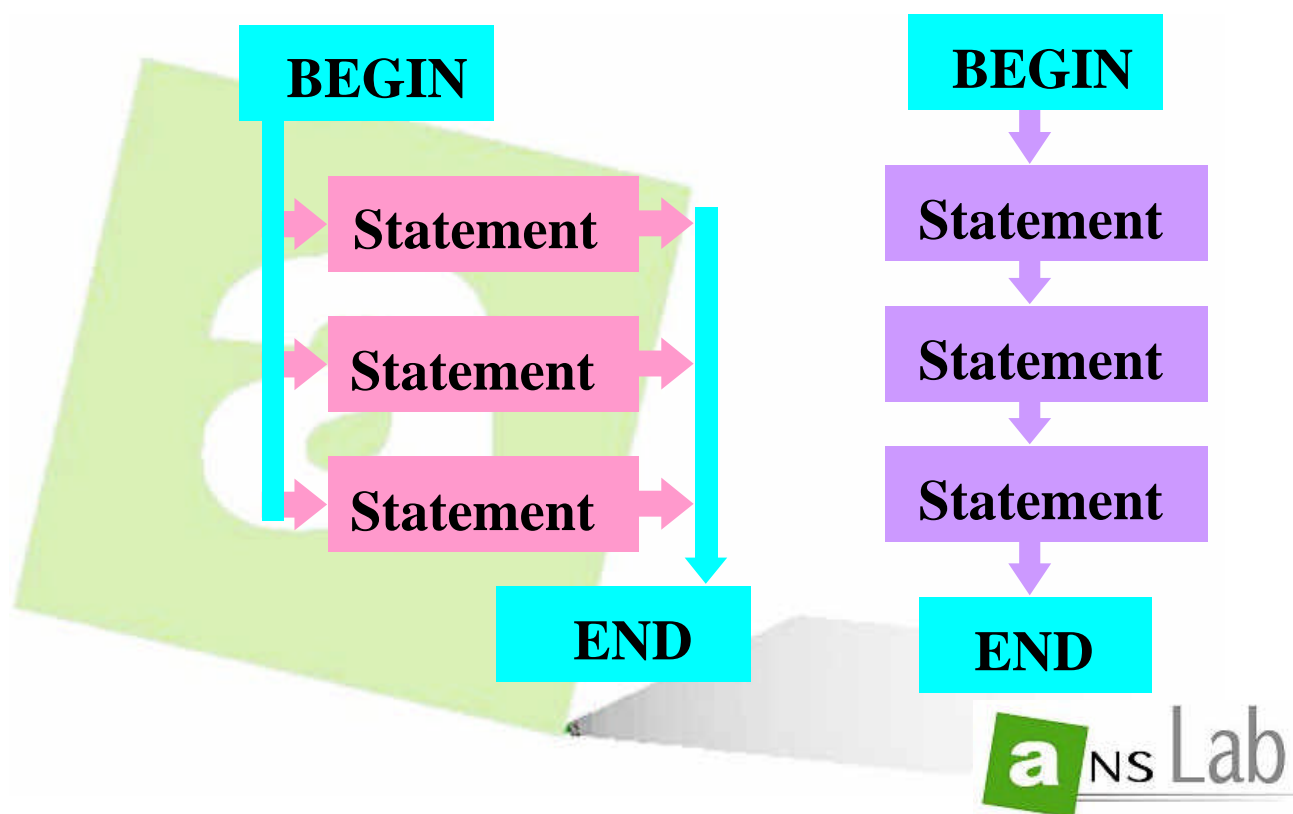

# Process Example

```
Entity experiment is
  port ( source : in bit_vector(0 to 3);
        ce : in bit;
        wrclk : in bit;
        selector : in bit_vector(0 to 1);
        result : out bit );
end experiment;

architecture behave od experiment is
  signal intreg : bit_vector(0 to 3);
begin -- dataflow(concurrent) environment
```

```
  writer : process -- process statement
    -- variable declarative region (empty here)
  begin
    -- sequential (clocked) statement
    wait until wrclk' event and wrclk='1' ;
    if (ce='1') then
      intreg <= source;
    end if;
  end process;
```

```
  reader : process (intreg, selector) -- process
    -- with sensitivity list
    -- variable declarative region (empty here)
  begin
    -- sequential (not-clocked) statements
    case selector is
      when "00" =>
        result <= intreg(0);
      when "01" =>
        result <= intreg(1);
      when "10" =>
        result <= intreg(2);
      when "11" =>
        result <= intreg(3);
    end case;
  end process;
```

```
end behave;
```



# Block Example

```
Architecture dataflow of example is
  signal global_sig, g1, g2, c, bit;
begin
```

```
  B1 : block -- Block declarative region
    signal local_sig : bit; -- Local SIGNAL
  begin -- Block concurrent statements

    local_sig <= global_sig; -- Communicate with global signal directly
```

```
  B2 : blobk (c='1') -- Block in a Block
    -- Block has "GUARD" expression
    port ( o1, o2 : out bit) -- Block port declarations
    port map (o1=>g1, o2=>g2); -- Block port mapping to global signal
  begin
    o1 <= guarded local_sig; -- Latch inference
    o2 <= global_sig
  end block;
```

```
end block;
```

```
end dataflow;
```



## Subprograms : Functions & Procedures

- Execute Sequentially
- Local variable
- Can be called from the dataflow (concurrent) or any sequential environment
- Can be overloaded (Synthesizer resolve this)
- Functions
  - all input argument, return single value
- Procedure
  - in, out, inout argument
  - Side effect



## Subprogram Example

```
■ Procedure
procedure increment ( vect : inout bit_vector; ena : in bit := '1' ) is -- in, inout argument
begin
  if (ena='1') then
    vect := vector_adder (x=>vect, "000001" ) ; -- Cause side effect
  end if ;
end increment ;
```

```
■ Functions
function vector_adder ( x : bit_vector; y : bit_vector) -- input argument
return bit_vector is -- return type
  variable carry : bit := '0' ;
  variable result : bit_vector(x' RANGE) ;
begin
  for i in x' RANGE loop
    result (i) := x(i) XOR y(i) XOR carry ;
    carry := carry AND (x(i) OR y(i)) OR x(i) AND y(i) ;
  end loop ;
  return result ; -- one return value
end vector_adder ;
```

## VHDL Objects

---

SIGNAL  
CONSTANT  
VARIABLE  
PORT  
Loop Variable  
Generic

## SIGNAL

---

- **Wire in a Logic Circuit**
- **CANNOT be declared in Sequential Blocks; “Function”, “Procedure” and “Process”**
- **Range restriction**
- **Initial value (but ignored by synthesis)**
- **Signal has Attribute; 'EVENT**
- **Assignment (<=) is scheduled after delta delay**

# VARIABLE

---

- **CANNOT** be declared in the dataflow(concurrent block) or Package
- Declared in Process, Function, and Procedure
- Initial value (but ignored by synthesis)
- Assignment (:=) is immediate



# CONSTANT

---

- **CANNOT** be assigned after declaration
- Initialization is required

```
constant ZEE_8 : std_logic_vector (0 to 7) := "ZZZZZZZZ";
```



# PORT

- **Interface terminal of Entity**
- **Normal signal with Direction Mode restriction:**
  - **IN, OUT : unidirectional**  
`s_out <= s_in1 + s_in0;`
  - **INOUT : bidirectional**  
`s_inout <= s_in1 + s_in0;`  
`s_out <= s_inout + s_in1;`
  - **BUFFER : bidirectional**  
`buff <= buff + s_in;`
- **CAN have initial value**



# GENERIC

- **Property of Entity**
- **Definition size of interface and Delay,etc.**

```
entity counter is
  generic ( size : integer := 8;
            delay : time := 10 ns; );
  port ( clk, reset : IN std_logic;
         count : OUT std_logic_vector( size-1 downto 0 ) );
end counter;
```

```
inst_1 : counter
  generic map (size => 16, delay => 5 ns)
  port map (clk=>clk, reset=>reset, count=>count);
```



## Loop Variable

---

- NOT declared
- Get its type and value from specified range in the iteration scheme

```
for i in 0 to (b' LENGTH-1) loop  
  a(i) <= b(i) and ena;  
end loop;
```



## VHDL Statements

---

Conditional Statements  
Selection Statements  
Loop and Generate Statements  
Assignment Statements



## Conditional Statements

### Dataflow

```
output_signal <=
    x when a=1 else
    y when a=2 else
    z when a=3 else
    (others=>"0");
```

### Behavior

```
if a=1 then
    output_signal <= x;
elsif a=2 then
    output_signal <= y;
elsif a=s then
    output_signal <= z;
else
    output_signal <= (others=>"0");
```



## Selection Statements

### Dataflow

```
with sel select
    output_signal <=
        x when "0010",
        y when "0100",
        z when "1000",
        (others=>"0")
        when others;
```

### Behavior

```
case sel is
    when "0010" =>
        output_signal <= x;
    when "0100" =>
        output_signal <= y;
    when "1000" =>
        output_signal <= z;
    when others =>
        output_signal <=
            (others=>"0");
end case;
```



## for / while loop statements

- Iterative/Repetitive operation
- Loop statement can be only used in sequential block (behavior)

```
-- for loop : Synthesizable
signal result, input_sig : bit_vector( 0 to 5);
signal ena;
.....
for i in 0 to 5 loop
    result(i) <= input_sig(i) and ena;
end loop;
```

```
-- while loop : partially synthesizable
variable i : integer;
.....
i := 0;
while ( i < 6 ) loop
    result(i) <= input_sig(i) and ena;
    i := i + 1;
end loop;
```



## for / while loop statements

- Sequential environment allow EXIT/NEXT statement in the Loop
- while loop is NOT synthesizable, if loop condition is evaluate at run-time

How many Loop ?

Synthesizer

How many bits of Hardware?

```
i := -1;
while (TRUE) loop
    i := i + 1;
    exit if ( i > 5 );
    if ( input_sig(i) = '0' ) then
        result(i) <= '0';
        next;
    end if;
    result(i) <= ena;
end loop;
```

*Synthesizable  
But NOT RECOMENDED style*



## for - generate loop

---

- Generate block execute concurrently
- NOT allow NEXT/EXIT statement
- Synthesizable

```
-- for-generate : Synthesizable  
signal result, input_sig : bit_vector( 0 to 5);  
signal ena;  
.....  
for i in 0 to 5 generate  
    result(i) <= input_sig(i) and ena;  
end generate;
```



## VHDL Assignment

---

SIGNAL      VARIABLE

## Concurrent/Sequential Assignment

- **SIGNAL**

- ┆ (concurrent statement)

- **VARIABLE**

- ┆ (sequential statement) : **PROCESS**

- **CONSTANT**

- ┆ **C** #define, Assembly

- ┆ **EQU**



## VARIABLE

- **VARIABLE :**

- ┆ “:=”

- ┆ (instaneous assignment)

- ┆ **PROCESS BLOCK** sequential statement

- ┆ **Example:**

- ┆ **AV := X\*Y;**

- ┆ **BV := AV+Z;**



# SIGNAL

## ■ SIGNAL :

- “<=”
- (delayed assignment)
- Concurrent statement
- Attributes
- Example:
  - AS <= X\*Y after 2 ns;
  - BS <= AS + Z after 2 ns;



# Assignment Execution

AS <= X \* Y after 2 ns;  
BS <= AS + Z after 2 ns;

AV := X \* Y;  
BV := AV + Z;

	Initial	T1	T1+2	T1+4	T1+6
X	1	4	5	5	3
Y	2	2	2	3	2
AS	2	2	8	10	15
Z	0	3	2	2	2
BS	2	2	5	10	12

*Delayed Concurrent Assignment*

	Initial	T1	T1+2	T1+4	T1+6
X	1	4	5	5	3
Y	2	2	2	3	2
AV	2	8	10	15	6
Z	0	3	2	2	2
BV	2	11	12	17	8

*Instantaneous Sequential Assignment*




# SIGNAL VARIABLE

```
ENTITY sigvar1 IS
  PORT(
    clk : IN std_logic;
    din : IN std_logic_vector(2 DOWNTO 0);
    dout : OUT std_logic_vector(2 DOWNTO 0) );
END sigvar1;
```



 
# SIGNAL VARIABLE (1)

```
ARCHITECTURE a_sigvar1 OF sigvar1 IS
  SIGNAL sig0, sig1 : std_logic_vector(2 DOWNTO 0);
BEGIN
  PROCESS (clk)
  BEGIN
    IF clk='1' AND clk'EVENT THEN
      sig0 <= din;
      sig1 <= sig0;
      dout <= sig1;
    END IF;
  END PROCESS;
END a_sigvar1;
```


 
## SIGNAL VARIABLE (2)

```
ARCHITECTURE a_sigvar2 OF sigvar2 IS
SIGNAL sig0, sig1 : std_logic_vector(2 DOWNTO 0);
BEGIN
PROCESS (clk)
BEGIN
IF clk='1' AND clk'EVENT THEN
  sig0 <= din; -- This statement infer F/F
  sig1 <= sig0; -- This statement infer another F/F
END IF;
END PROCESS;
dout <= sig1; -- "sig1" DOES NOTHING. Just Connected to "dout"
END a_sigvar2;
```



## SIGNAL VARIABLE (2-1)


```
ARCHITECTURE a_sigvar2_1 OF sigvar2_1 IS
SIGNAL sig0, sig1 : std_logic_vector(2 DOWNTO 0);
BEGIN
PROCESS (clk)
BEGIN
IF clk='1' AND clk'EVENT THEN
  sig0 <= din; -- This Statement infers F/F
END IF;
END PROCESS;
sig1 <= sig0; -- This is Concurrent assignment
dout <= sig1; -- "sig0" and "sig1" is does NOTHING! Just Connected
END a_sigvar2_1;
```

## SIGNAL VARIABLE (3)

```

ARCHITECTURE a_sigvar3 OF sigvar3 IS
  SIGNAL sig0, sig1 : std_logic_vector(2 DOWNTO 0);
BEGIN
  PROCESS (clk)
  BEGIN
    IF clk='1' AND clk'EVENT THEN
      sig1 <= sig0; -- Concurrent assignment in the Process Block does
      sig0 <= din; -- not cares it's sequence. Compare Example #2
    END IF;
  END PROCESS;
  dout <= sig1;
END a_sigvar3;

```

 


## SIGNAL VARIABLE (4)

```

ARCHITECTURE a_sigvar4 OF sigvar4 IS
BEGIN
  PROCESS (clk)
  VARIABLE var0, var1 : std_logic_vector(2 DOWNTO 0);
  BEGIN
    IF clk='1' AND clk'EVENT THEN
      var0 := din; -- These two sequential assignment DOES NOTHING!
      var1 := var0; -- Compare with Concurrent assignment; Example #2 and #3
      dout <= var1; -- Just this statement infers F/F between "din" and "dout"
    END IF;
  END PROCESS;
END a_sigvar4;

```

 




# SIGNAL VARIABLE (5)

```

ARCHITECTURE a_sigvar5 OF sigvar5 IS
BEGIN
  PROCESS (clk)
    VARIABLE var0, var1 : std_logic_vector(2 DOWNTO 0);
    BEGIN
      IF clk='1' AND clk'EVENT THEN
        var1 := var0; -- These Two sequential statement infer TWO stage F/F
        var0 := din; -- The order of Sequential statements are very important!
                      -- Compare with Example #4
        dout <= var1; -- F/F inferred between "var0" and "dout"
                      -- Another F/F is inferred between "din" and "var0"
      END IF;
    END PROCESS;
  END a_sigvar5;

```

 *These Two sequential statement infer TWO stage F/F*  
*The order of Sequential statements are very important!*  
*Compare with Example #4*  
*F/F inferred between "var0" and "dout"*  
*Another F/F is inferred between "din" and "var0"*



# SIGNAL VARIABLE (6)

```


ARCHITECTURE a_sigvar5 OF sigvar5 IS
BEGIN
  PROCESS (clk)
    VARIABLE var0, var1 : std_logic_vector(2 DOWNTO 0);
    BEGIN
      IF clk='1' AND clk'EVENT THEN
        var0 := din; -- Synthesized as ONE stage F/F
        var1 := var0; -- between "din" and "var1"
      END IF;
      dout <= var1; -- But "var1" does nothing!, connected to "dout"
                  -- F/F inferred between "din" and "dout"
    END PROCESS;
  END a_sigvar5;

```

*VARIABLEs are "local"*

*Pass local VARIABLE to global SIGNAL*

 *Synthesized as ONE stage F/F*  
*between "din" and "var1"*  
*But "var1" does nothing!, connected to "dout"*  
*F/F inferred between "din" and "dout"*



# SIGNAL VARIABLE (7)

```

ARCHITECTURE a_sigvar7 OF sigvar7 IS
BEGIN
  PROCESS (clk)
  VARIABLE var0 : std_logic_vector(3 DOWNT0 0);
  BEGIN
    var0 := "0000"; -- These Three sequential statement
    var0(3) := '1'; -- builds Bit map "1010"
    var0(1) := '1';
    IF clk='1' AND clk'EVENT THEN
      dout <= var0 AND din;
    END IF;
  END PROCESS;
END a_sigvar7;

```

*Sequential assignment has NO multiple drive*

*Bit 1, 3 inferred F/F*

*Bit 0, 2 always '0'*

# SIGNAL VARIABLE (8)

```

ARCHITECTURE a_sigvar7 OF sigvar7 IS
  SIGNAL sig0 : std_logic_vector(3 DOWNT0 0);
  BEGIN
    PROCESS (clk)
    BEGIN
      sig0 <= "0000"; -- The concurrent statement in the PROCESS block
      sig0(3) <= '1'; -- works sequentially...
      sig0(1) <= '1'; -- Compare with Example #7
      IF clk='1' AND clk'EVENT THEN
        dout <= sig0 AND din;
      END IF;
    END PROCESS;
  END a_sigvar7;

```

*Sequential Block : NO multiple drive problem*

*Concurrent NOT allow multiple drive!*

*Following concurrent Statements cause MULTIPLE Drive ERROR!  
This region is CONCURRENT!!!!!!!!!!!!!!*

*-- sig0 <= "0000";  
-- sig0(3) <= '1';  
-- sig0(1) <= '1';*

## VHDL Operator

---

IEEE 1076 Predefined  
IEEE 1164 Predefined  
Synthesizable Arithmetics  
Operator Overloading

## VHDL Operators (IEEE 1076)

---

- **Binary operators:**
  - AND, OR, NAND, NOR, XOR, NOT
  - predefined for BIT and BOOLEAN
- **Relational operators:**
  - =, /=, <, >, <=, >=
  - predefined for all types
- **Arithmetic operators:**
  - +, -, \*, /, \*\*, abs, mod, rem
  - predefined for integer types
- **Concatenation operators:**
  - &

# Synthesizable Arithmetic Operators

## IEEE 1076.3 Arithmetic Package

### std\_logic\_1164 Package

- | New Logic types : std\_logic, std\_ulogic

- | Logical Operators

### numeric\_bit

- | +, -, \*,abs between SIGNED, UNSIGNED of bit and bit\_vector

### numeric\_std

- | +, -, \*,abs between SIGNED, UNSIGNED of std\_logic and std\_logic\_vector

## Synopsys Arithmetic Package

### std\_logic\_arith

### std\_logic\_signed

### std\_logic\_unsigned



# AND Operator (IEEE 1164)

```
-- truth table for "and" function
CONSTANT and_table : stdlogic_table := (
-----
-- | U X 0 1 Z W L H - | |
-----
( 'U', 'U', '0', 'U', 'U', 'U', '0', 'U', 'U' ), -- | U |
( 'U', 'X', '0', 'X', 'X', 'X', '0', 'X', 'X' ), -- | X |
( '0', '0', '0', '0', '0', '0', '0', '0', '0' )
( 'U', 'X', '0', '1', 'X', 'X', '0', '1', 'X' ) -- and
( 'U', 'X', '0', 'X', 'X', 'X', '0', 'X', 'X' )
( 'U', 'X', '0', 'X', 'X', 'X', '0', 'X', 'X' )
( '0', '0', '0', '0', '0', '0', '0', '0', '0' )
( 'U', 'X', '0', '1', 'X', 'X', '0', '1', 'X' )
( 'U', 'X', '0', 'X', 'X', 'X', '0', 'X', 'X' )
);

FUNCTION "and" ( l,r : std_logic_vector ) RETURN std_logic_vector IS
  ALIAS lv : std_logic_vector ( 1 TO l'LENGTH ) IS l;
  ALIAS rv : std_logic_vector ( 1 TO r'LENGTH ) IS r;
  VARIABLE result : std_logic_vector ( 1 TO l'LENGTH );
BEGIN
  IF ( l'LENGTH /= r'LENGTH ) THEN
    ASSERT FALSE
    REPORT "arguments of overloaded 'and' operator are not of the same length"
    SEVERITY FAILURE;
  ELSE
    FOR i IN result'RANGE LOOP
      result(i) := and_table (lv(i), rv(i));
    END LOOP;
  END IF;
  RETURN result;
END "and";
```

## Synthesizable Arithmetic Operators

### ■ IEEE 1076.3

- Accepted types : “SIGNED”, “UNSIGNED”, NATURAL, INTEGER
- Use Type Conversion for STD\_LOGIC
- Types defined (NUMERIC\_STD)
  - type UNSIGNED is array (NATURAL range <>) of STD\_LOGIC;
  - type SIGNED is array (NATURAL range <>) of STD\_LOGIC;
- Types defined (NUMERIC\_BIT)
  - type UNSIGNED is array (NATURAL range <> ) of BIT;
  - type SIGNED is array (NATURAL range <> ) of BIT;
- Validation Suit



## Synthesizable Arithmetic Operators

### ■ Arithmetic Operators

- Built-in Subprogram
- In-Fix
  - + , - , / , \* , = , /= , < , > , <= , >= , rem , mod
  - Synthesizer NOT support “/”, “rem”, “mod”
- Unary
  - abs , -

### ■ Edge Detection (NUMERIC\_BIT)

- RISING\_EDGE
- FALLING\_EDGE



## Synthesizable Arithmetic Operators

### ■ SHIFT/ROTATE

- SHIFT\_RIGHT, SHIFT\_LEFT
- ROTATE\_RIGHT, ROTATE\_LEFT

### ■ Type Conversion

- RESIZE
- TO\_INTEGER, TO\_UNSIGNED, TO\_SIGNED

### ■ Logical Operations

- NOT, OR, NOR, AND, NAND, XNOR



## Synthesis Example (Synopsys Library)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;      -- Synopsys Arithmetic Package
use ieee.std_logic_unsigned.all;  -- Synopsys Arithmetic Package

architecture behave of prep5 is
    signal q_i, adder_output, multiply_output: std_logic_vector (7 downto 0);
begin
    multiply_output <= a * b;      -- STD_LOGIC_VECTOR Type Multiply/Addition
    adder_output <= (multiply_output + q_i) when mac = '1' else
        multiply_output;
    .....
end behave;
```



## Synthesis Example (IEEE 1076.3)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all; -- IEEE 1076.3 Synthesis Library

architecture behave of prep5 is
    signal q_i, adder_output, multiply_output: unsigned (7 downto 0);
    -- Unsigned SIGNAL

begin
    multiply_output <= signed(a) * signed(b); -- Convert to STD_LOGIC
    -- to UNSIGNED


    adder_output <= (multiply_output + q_i) when mac = '1' else
        multiply_output;

    q <= std_logic_vector(adder_output); -- Interface to STD_LOGIC
end behave;
```


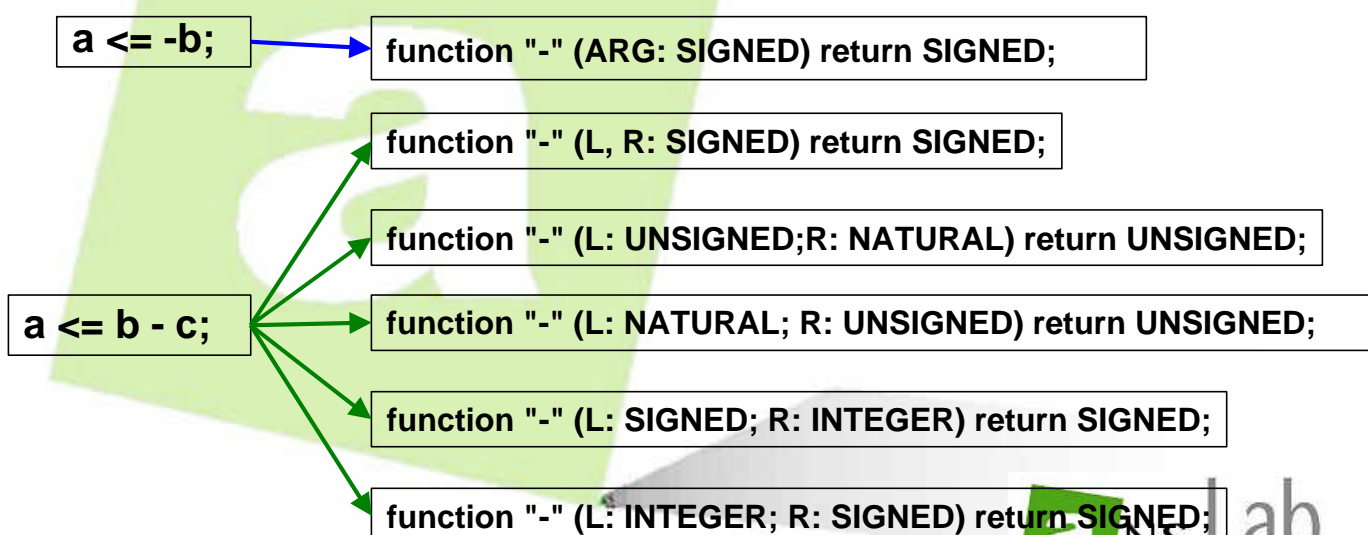
## Operator Overloading

- VHDL is Object-Oriented
- Type check strictly, but Overloading



## VHDL Attributes

---

Predefined Attributes  
Vendor-Defined Attributes  
Tool-Defined Attributes

## Attributes

---

- **Predefined attributes**
  - Return information about data types, signals, blocks, architectures, events, etc.
  - Examples: 'LENGTH, 'LEFT, 'EVENT
- **Vendor defined attributes**
  - Often used in synthesis
  - Example: enum\_encoding, pinnum
- **User defined attributes**
  - Not often used



## VHDL Predefined Attributes

- Defined for SIGNAL
- Edge of SIGNAL
  - EVENT
- Value Returning
  - LEFT
  - RIGHT
  - HIGH
  - LOW
  - LENGTH
  - RANGE
  - REVERSE\_RANGE



## Predefined Attribute Example

```
signal vector_up : bit_vector( 4 to 9);
signal vector_dn : bit_vector( 25 to 0);

vector_up' LEFT -- returns integer 4
vector_dn' LEFT -- returns integer 25
vector_up' RIGHT -- returns integer 9
vector_dn' RIGHT -- returns integer 0
vector_up' HIGH -- returns integer 9
vector_dn' HIGH -- returns integer 25
vector_up' LOW -- returns integer 4
vector_dn' LOW -- returns integer 0
vector_up' LENGTH -- returns integer 6
vector_dn' LENGTH -- returns integer 26
vector_up' RANGE -- returns integer range 4 to 9
vector_dn' RANGE -- returns integer range 25 to 0
vector_up' REVERSE_RANGE -- returns integer range 9 to 4
vector_dn' REVERSE_RANGE -- returns integer range 0 to 25
```



## Vendor-Defined Attributes

### ■ Metamor Synthesizer

#### ■ Pin Number Attribute

```
ENTITY test IS
  PORT ( clk, start : IN bit;
        count0, count1 : out bit );
  attribute pinnum : string; -- define pinnum attribute
  attribute pinnum of clk : signal is "13";
  attribute pinnum of start : signal is "8";
  attribute pinnum of seg40 : signal is "19";
  attribute pinnum of seg41 : signal is "20";
END test;
```



## User Defined Attributes

### ■ Why?

#### ■ Example

```
signal my_vector : bit_vector (0 to 4);
attribute MIDDLE : integer;
attribute MIDDLE of my_vector : signal is my_vector' LENGTH/2;
.....
my_vector' MIDDLE -- returns integer 2
```



## Usage of Attributes (Example)

```
Entity masked_parity is
  generic ( size: integer :=5);
  port ( source : in bit_vector(0 to size);
        mask : in bit_vector(source' RANGE); -- RANGE (0 to size)
        result : out bit );
end masked_parity;

architecture behave of masked_parity is
begin
  process (source, mask)
    variable tmp : bit;
    variable masked_source : bit_vector (source' RANGE); -- RANGE (0 to size)
  begin
    masked_source := source and mask;
    tmp := masked_source(source' LEFT); -- LEFT
    for I in source' LEFT+1 to source' RIGHT loop -- RIGHT
      tmp := tmp xor masked_source(I);
    end loop;
    result <= tmp;
  end process;
end behave;
```



## Usage of Attribute (Example)

```
function TO_INTEGER (ARG: UNSIGNED) return NATURAL is
  constant ARG_LEFT: INTEGER := ARG'LENGTH-1; -- LENGTH
  alias XARG: UNSIGNED(ARG_LEFT downto 0) is ARG;
  variable RESULT: NATURAL := 0;
begin
  if (ARG'LENGTH < 1) then
    assert NO_WARNING
    report "NUMERIC_BIT.TO_INTEGER: null detected, returning 0"
    severity WARNING;
    return 0;
  end if;
  for I in XARG'RANGE loop -- RANGE
    RESULT := RESULT+RESULT;
    if XARG(I) = '1' then
      RESULT := RESULT + 1;
    end if;
  end loop;
  return RESULT;
end TO_INTEGER;
```



## BUS and REGISTER

---

## BUS and REGISTER

---

- **VHDL Entity Class**

- **BUS**

- | make GUARDED signal (three-state)

- **REGISTER**

- | make Latch inference

## BUS Example

```
-- include the IEEE 1164 package to use type std_logic.
library ieee ;
use ieee.std_logic_1164.all ;

entity test_bus is
  port ( c,d : std_logic ;
        o : out std_logic BUS) ; -- An entity with a BUS entity-class signal
end test_bus ;

architecture behave of test_bus is
begin
  process (c,d)
  begin
    if (c = '1') then
      o <= d ;
    else
      o <= NULL ; -- Switch-Off (Three-State)
    end if ;
  end process ;
end behave ;
```



## REGISTER Example

```
-- include the IEEE 1164 package to use type std_logic.
library ieee ;
use ieee.std_logic_1164.all ;

entity test_reg is
  port ( c,d : std_logic ;
        o : out std_logic);
end test_reg ;

architecture behave of test_reg is
  signal s_o : std_logic REGISTER; -- REGISTER entity-class signal
begin
  process (c,d)
  begin
    if (c = '1') then
      s_o <= d ;
    else
      s_o <= NULL ; -- DO NOTHING, Latch inference
    end if ;
  end process ;
  o <= s_o;
end behave ;
```



## VHDL Synthesis

---

Flip-Flops  
Three-,Bi-Dir Buffers  
State Machines  
Arithmetic and Related Logics  
Resource Sharing and Optimization  
Mux and Selectors  
ROM, PLA, Decoders

## Goals of This Section


---

- **More closely examine synthesis conventions**
- **Find out what is and is not synthesizable in today's tools**
- **See how HDL statements relate to actual hardware**
- **Examine the most common synthesis pitfalls**


## Flip-Flops

Sync/Async Rest or Reset  
Latch  
Chip Enable

## Flip-Flop Convention

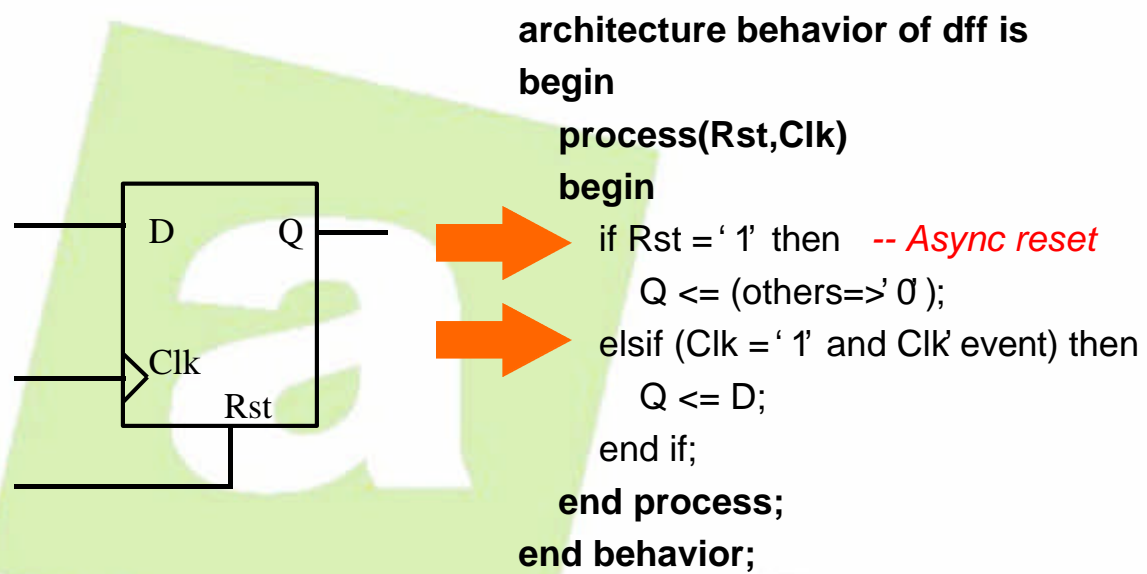

## Synchronous Reset Convention

 


architecture behavior of dff is

```
begin
process(Clk)
begin
if (Clk = '1' and Clk' event) then
if Rst = '1' then -- Sync reset
Q <= (others=>'0');
else
Q <= D;
end if;
end if;
end process;
end behavior;
```

**a**NS Lab

## Latch Convention

 


architecture behavior of latch is

```
begin
process(LE, D)
begin
if LE = '1' then
Q <= D;
end if;
end process;
end behavior;
```

**a**NS Lab



# Clock Enable

 

architecture behavior of dff is

```
begin
process(Clk)
begin
if Clk = '1' and Clk' event then
if CE = '1' then
Q <= D;
end if;
end if;
end process;
end behavior;
```



# Flip-Flop Convention (block)


```
-- Level Sensitive
B1 : block (ena='1')
begin
Q <= guarded D;
end block;
```

```
-- Edge-Sensitive Sync reset
B2 : block (clk' event and clk='1')
begin
Q <= guarded 0 when Rst='1' else D;
end block;
```

```
-- Clock Enable
B2 : block (clk' event and clk='1')
begin
Q <= guarded D when CE='1' else Q;
end block;
```



## Gated Clock

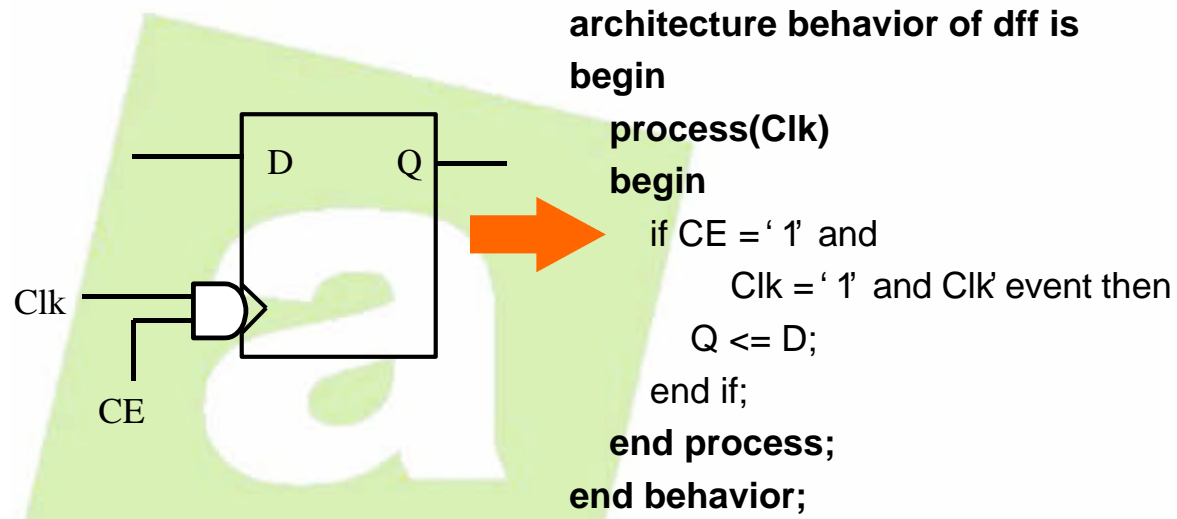

**a**NS Lab

## Flip-Flop (Wait Statement)

```
architecture behavior of dff is
begin
  process ← NO Sensitivity List
  begin
    wait until clk' event and clk='1'; ←
    Q <= D;
  end process;
end behavior;
```

**a**NS Lab

## Suggested Register Conventions

---

- Use a **process** statement (or procedure) to describe a flip-flop or latch
- Use **'event** attribute or **rising\_edge** function to detect clock edge
- Use **if-then-else** style for reset and clock logic
- **Avoid Gated Flip-Flop**
- **Avoid accidental Latch**
- **Verilog conventions are similar**



## Buffers

---

Three-State Buffers  
Bi-Directional Buffers  
Buses

# Three-state Buffers

```
entity three-state is
port ( input_1, input_2 : in std_logic ;
      ena_1, ena_2 : in std_logic ;
      output : out std_logic ) ;
end three-state ;
```

```
architecture dataflow of three-state is
begin
```

*-- Dataflow*

```
output <= input_1 when ena_1 = '1' else 'Z' ;
output <= input_2 when ena_2 = '1' else 'Z' ;
```

```
end dataflow ;
```

*-- Behavior*

```
driver1 : process (ena_1, input_1)
begin
if (ena_1='1') then
output <= input_1 ;
else
output <= 'Z' ;
end if ;
end process ;
```

```
driver2 : process (ena_2, input_2)
begin
if (ena_2='1') then
output <= input_2 ;
else
output <= 'Z' ;
end if ;
end process ;
```

*Multiple Drive!*

*Synthesizable, but "ena\_1" and "ena\_2"  
Never be '1' simultaneously!*



# Bi-Directional Buffers

```
entity bidir_function is
port ( bidir_port : inout std_logic ;
      ena         : in std_logic ;
      ...
      ) ;
end bidir_function ;
```

```
architecture a_bidir of bidir_function is
signal internal_signal, internal_input : std_logic ;
begin
```

```
bidir_port <= internal_signal when ena = '1' else 'Z' ;
internal_input <= bidir_port ;
```

```
-- use internal_input
..... <= internal_input;
```

```
-- generate internal_signal
internal_signal <= .....
```

```
end a_bidir ;
```



# Buses

---

```
entity three-state is
  port ( input_signal_1, input_signal_2 : in  std_logic_vector (0 to 7) ;
        ena_1, ena_2 : in  std_logic ;
        output_signal : out std_logic_vector(0 to 7)
  );
end three-state ;

architecture exemplar of three-state is
begin

  output_signal <= input_signal_1 when ena_1 = ' 1' else ' ZZZZZZZZ ;
  output_signal <= input_signal_2 when ena_2 = ' 1' else ' ZZZZZZZZ ;

end exemplar ;
```




# State Machine


---

## Moore/Mealy Machine

### Moore Machine

 

### Mealy Machine

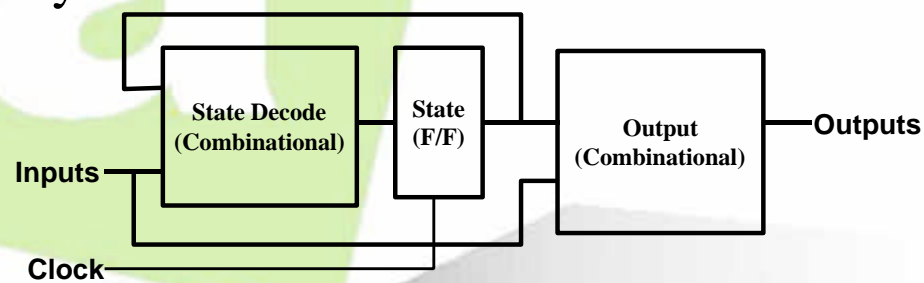

**a**NS Lab

## State Machine Coding Style

- Use Enumeration Type to represent “State”
- Supply Power-Up and Reset Condition
- Use **case** statement for state transition
- DO NOT use **OTHER** entry in the **case**
- Use **if~else** for input condition
- Always assign state output under every condition

**a**NS Lab

# State Machine Example

## DRAM Refresh

```
entity ras_cas is
  port ( clk, cs, refresh, reset : in bit ;
        ras, cas, ready       : out bit ) ;
end ras_cas ;
```

```
architecture a_ras_cas of ras_cas is
```

```
-- Define the possible states of the state machine
```

```
type state_type is (s0, s1, s2, s3, s4) ;
```

```
signal present_state, next_state : state_type ;
```

```
begin
```

```
  registers : process (clk, reset)
```

```
  begin
```

```
    -- process to update the present state
```

```
    if (reset='1') then
```

```
      present_state <= s0 ;
```

```
    elsif clk' event and clk = '1' then
```

```
      present_state <= next_state ;
```

```
    end if ;
```

```
  end process ;
```

Enumerate Type

State F/F



# State Machine Example (cont.)

```
transitions :
```

```
process (present_state, refresh, cs)
```

```
begin
```

```
-- process to calculate the next state
```

```
-- and the outputs
```

```
case present_state is
```

```
  when s0 =>
```

```
    ras <= '1' ; cas <= '1' ; ready <= '1' ;
```

```
    if (refresh = '1') then
```

```
      next_state <= s3 ;
```

```
    elsif (cs = '1') then
```

```
      next_state <= s1 ;
```

```
    else
```

```
      next_state <= s0 ;
```

```
    end if ;
```

```
  when s1 =>
```

```
    ras <= '0' ; cas <= '1' ; ready <= '1' ;
```

```
    next_state <= s2 ;
```

```
  when s2 =>
```

```
    ras <= '0' ; cas <= '0' ; ready <= '0' ;
```

```
    if (cs = '0') then
```

```
      next_state <= s0 ;
```

```
    else
```

```
      next_state <= s2 ;
```

```
    end if ;
```

```
  when s3 =>
```

```
    ras <= '1' ; cas <= '0' ; ready <= '0' ;
```

```
    next_state <= s4 ;
```

```
  when s4 =>
```

```
    ras <= '0' ; cas <= '0' ; ready <= '0' ;
```

```
    next_state <= s0 ;
```

```
end case ;
```

```
end process ;
```

```
end a_ras_cas ;
```



# Arithmetic and Relational Logic

## Overview

- **VHDL Synthesizer Generate Arithmetic Logic**
  - Technology Specific Macros
  - Use Optimized Library of Parametized Module
  - Synthesizable operators : “+”, “-”, “\*”, “abs”
  - “-” apply same as “+”
  - “=”, “/=", “<”, “>”, “<=”, “>=” generate comparator
- **Avoid explosion of combinational logic**
  - Constant operand
  - Division(“/”) by power of two (Shifter)
  - Synthesizable exponentiation(“\*\*”), if both constant operands
- **Integer Operation**
  - Bit-width of generated arithmetic circuit is depend on operand’s range defined
  - 2’s complement implementation if integer range extends below 0
  - unsigned implementation, when positive range




# Arithmetic Logic (RTL View)

```

entity add_int8 is
  port(
    a, b : in integer range 0 to 15;
    c : out integer range 0 to 15
  );
end add_int8;

 architecture behave of add_int8 is
begin
  c <= a + b;
end behave;
  
```




Synthesis RTL View




# Arithmetic Logic (Tech. View)

## Altera Device

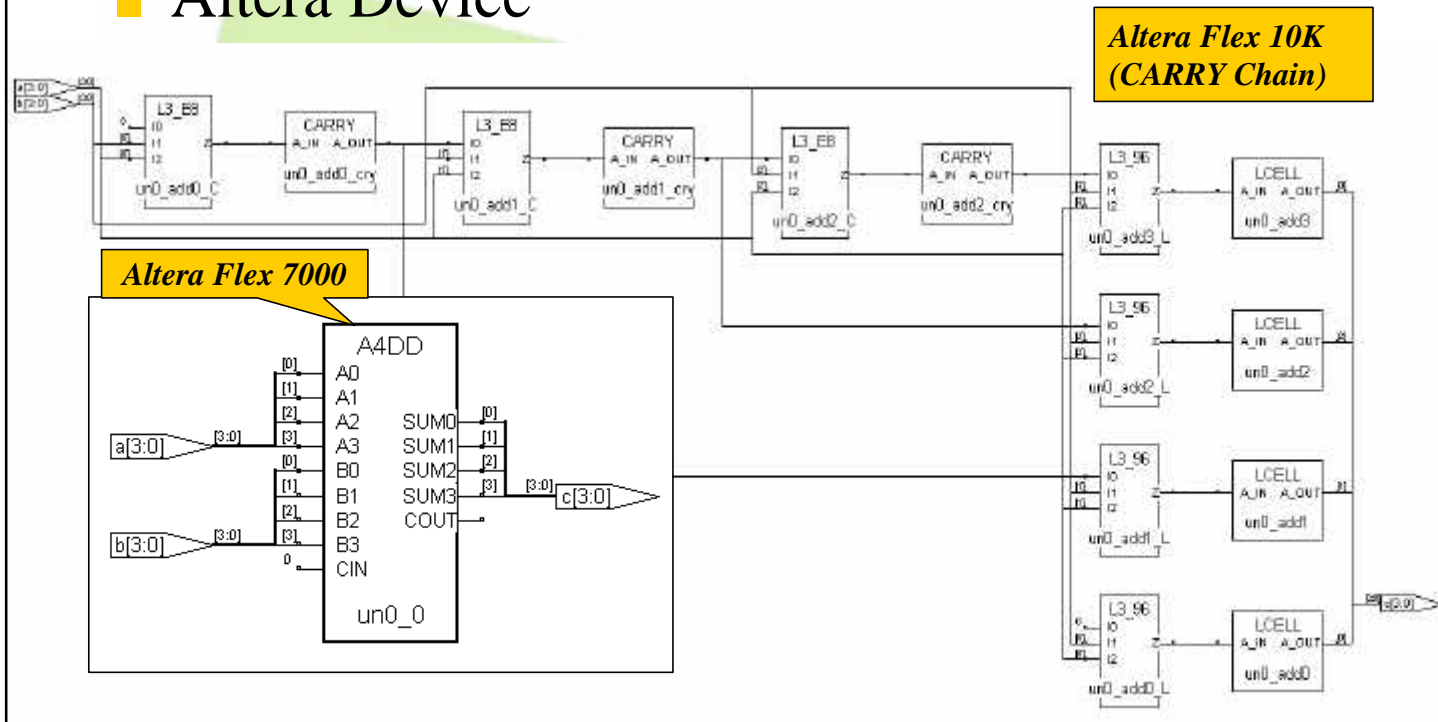

# Arithmetic Logic (Tech. View)

## Vantis Mach Device

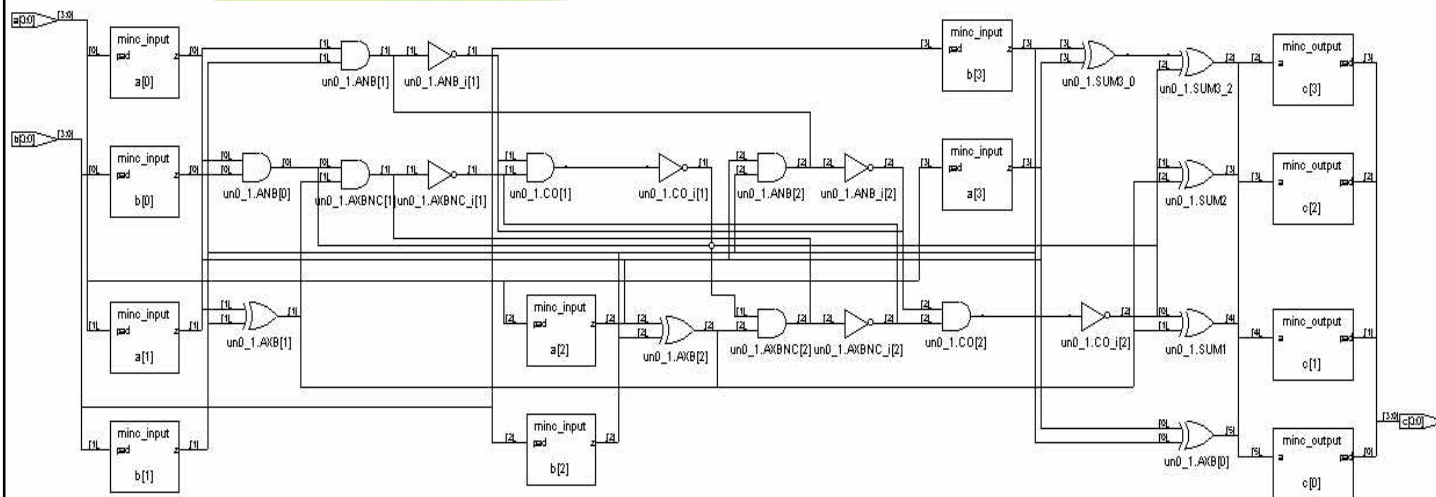

**a**NS Lab


# Integer Division Example (1)

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity div_posint is
    port( a : in integer range 0 to 255;
          c : out integer range 0 to 255 );
end div_posint;

 architecture behave of div_posint is
begin
    c <= a / 4;
end behave;
    
```




**a**NS Lab
 
## Integer Division Example (2)

```
entity div_cmpl is
  port( a : in integer range -128 to 127;
        c : out integer range -256 to 255 );
end div_cmpl;
```

```
architecture behave of div_cmpl is
begin
  c <= a / 4;
end behave;
```



## Improve Synthesis

- Module Generation
- Resource Sharing
- Ranged Integer
- Design Optimization

# Module Generation

- **Optimized generic modules (Parametized Library Modules)**
  - Memory Module : ROM, RAM
  - Counters
  - Arithmetic and Relational logic
- **Technology Specific Macros**
- **Mega/Macro Functions**
- **Most synthesizer tools support Technology specific macros and/or Module Generation options**



# LPM Package Example (Altera)

```
component LPM_ADD_SUB
  generic (
    LPM_WIDTH: positive;
    LPM_REPRESENTATION: string := SIGNED;
    LPM_DIRECTION: string := UNUSED;
    LPM_HINT : string := UNUSED;
    LPM_PIPELINE : integer := 0;
    LPM_TYPE: string := L_ADD_SUB );
  port (
    DATAA: in std_logic_vector(LPM_WIDTH-1 downto 0);
    DATAB: in std_logic_vector(LPM_WIDTH-1 downto 0);
    ACLR : in std_logic := '0';
    CLOCK : in std_logic := '1';
    CIN: in std_logic := '0';
    ADD_SUB: in std_logic := '1';
    RESULT: out std_logic_vector(LPM_WIDTH-1 downto 0);
    COUT: out std_logic;
    OVERFLOW: out std_logic );
end component;
```



## Device Specific Synthesis

- Specifying place-and-route constraints, etc. can be tricky in an HDL.
- Examples: pin assignments, critical nets, clock buffers, etc.
- Hierarchy can be used to reference non-VHDL elements in some tools.
- No standards have been established; follow your synthesis documentation!



## Pin Assignments

**Entity CONTROL Is**

**Port (Reset, Clk, Mode, VS, ENDFR: in std\_ulogic;**

**RAMWE, RAMOE: out std\_ulogic;**

**ADOE, INCAD: out std\_ulogic);**

attribute pinnum: string;

attribute pinnum of Clk: signal is "1"; *-- Device Specific !*

attribute pinnum of Mode: signal is "2";

attribute pinnum of Data: signal is "37,23,22,21,20,19,18,17";

attribute pinnum of Addr: signal is "29,28,27,26,16,25,24,12";

attribute pinnum of RAMWE: signal is "32";

attribute pinnum of RAMOE: signal is "33";

attribute pinnum of ADOE: signal is "34";

**End CONTROL;**



## Device-specific Macros

architecture structure of lca\_macro is

*-- Refer to vendor supplied Libraries*

```
component RAM16x1
  port (A0, A1, A2, A3, WE, D: in STD_LOGIC;
        O: out STD_LOGIC);
end component;
begin
  ...
  RAM1: RAM16x1 port map (A(0),A(1),A(2),A(3),WE,
                          DATAIN, DATAOUT) ;
  ...
end structure;
```



## Resource Share (use Temp signal)

```
process(a,b,c,d)
begin
  if ( a+b=c ) then
    e <= a;
  elsif ( a+b=d ) then
    e <= b;
  else
    e <= c;
  end if;
end process;
```

```
process(a,b,c,d)
variable temp : integer range 0 to 15;
begin
  → temp := a + b;
  if ( temp=c ) then
    e <= a;
  elsif ( temp=d ) then
    e <= b;
  else
    e <= c;
  end if;
end process;
```




## Resource Share (use parenthesis)

```

process(a,b,c,d)
begin
  e <= a + b + c;
  f <= b + c + d;
end process;
    
```

```

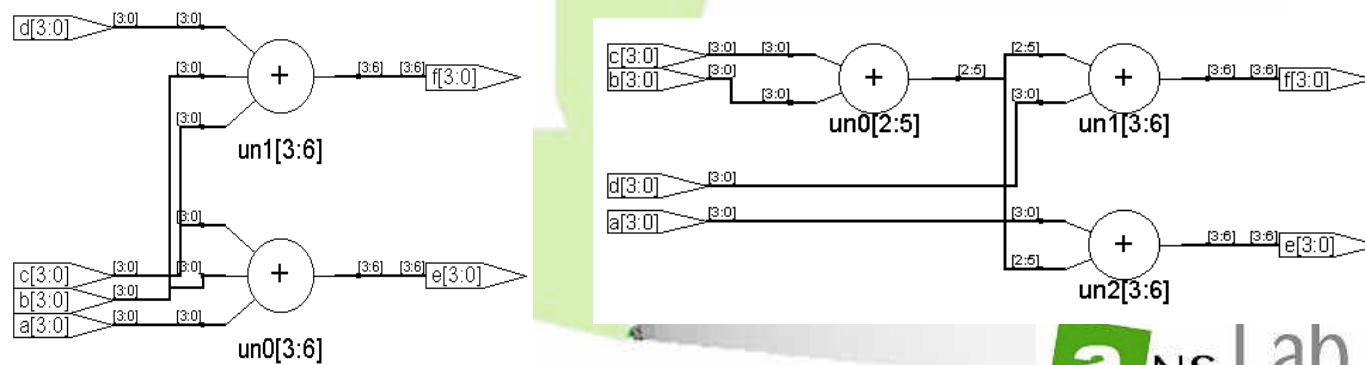process(a,b,c,d)
begin
  e <= a + (b + c);
  f <= (b + c) + d;
end process;
    
```



aNS Lab


## Resource Share (mutual exclusive)

```

process(a,b,c,test)
begin
  if (test=TRUE) then
    o <= a + b;
  else
    o <= a + c;
  end if;
end process;
    
```

```

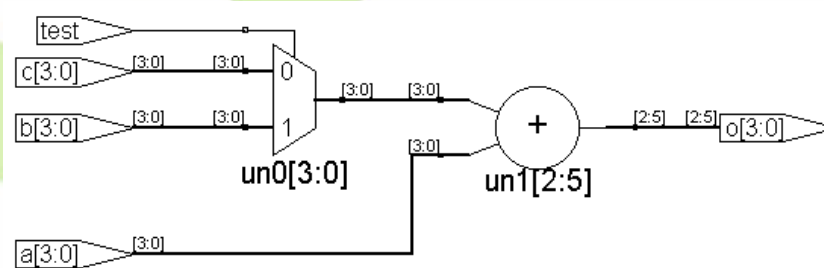process(a,b,c,test)
variable temp : integer range 0 to 15;
begin
  if (test=TRUE) then
    temp := b;
  else
    temp := c;
  end if;
  o <= a + temp;
end process;
    
```



aNS Lab

# Ranged Integer

- Integer type : 32-bit default

```
variable a, b, c : integer;  
c := a + b; -- 32-bit adder
```

- Ranged integer

```
variable a, b, c : integer range 0 to 255; ←  
c := a + b; -- 8-bit adder
```



# Advanced Design Optimization

- Change functionality without violating design spec.
- Understand VHDL and Circuit generated by Synthesizer
- Example : Loadable counter

```
L_count1 :  
process  
begin  
→ wait until clk'event and clk='1';  
if (count = value) then  
count <= 0;  
count_done <= TRUE;  
else  
count <= count + 1;  
count_done <= FALSE;  
end if;  
end process;
```


```
L_count2 :  
process  
constant ZERO : integer range 0 to 15 := 0;  
begin  
→ wait until clk'event and clk='1';  
if (count = ZERO) then  
count <= value;  
count_done <= TRUE;  
else  
count <= count - 1;  
count_done <= FALSE;  
end if;  
end process;
```






## Loadable counter

### L\_count1

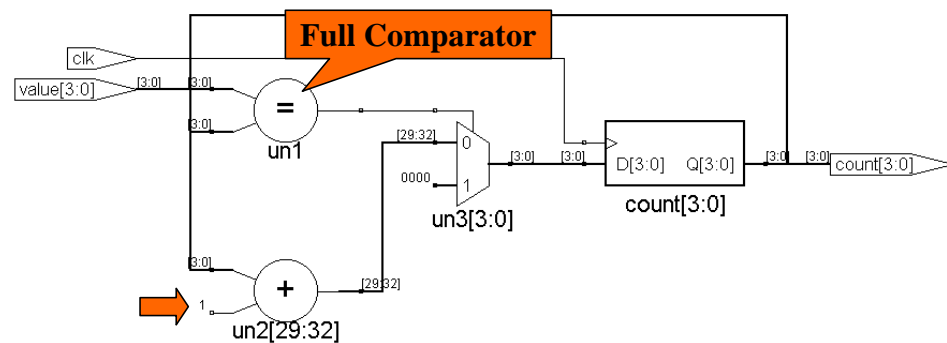

### L\_count2

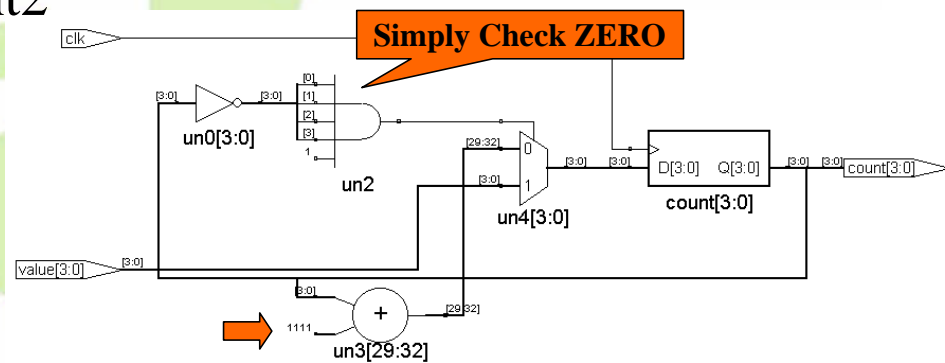

## Multiplexer and selectors

### Use case statement

```
case test_vector is
  when "000" => o <= bus(0) ;
  when "001" | "010" | "100" => o <= bus(1) ;
  when "011" | "101" | "110" => o <= bus(2) ;
  when "111" => o <= bus(3) ;
end case;
```

### Use variable indexed array

```
signal vec : std_logic_vector (0 to 15) ;
signal o : std_logic ;
signal i : integer range 0 to 15 ;
...
o <= vec(i) ;
```

*Equiv.*

```
case i is
  when 0 => o <= vec(0) ;
  when 1 => o <= vec(1) ;
  when 2 => o <= vec(2) ;
  when 3 => o <= vec(3) ;
  ...
end case ;
```

# ROMs, PLAs and Decoders

## ROM

- Address : case condition
- Data : case statement

```
case address is
  when "0000" => data <= "0111111";
  when "0001" => data <= "0011000";
  when "0010" => data <= "1101101";
  when "0011" => data <= "1111100";
  when "0100" => data <= "1011010";
  when "0101" => data <= "1110110";
  when "0110" => data <= "1110110";
  when "0111" => data <= "0011100";
  when "1000" => data <= "1111111";
  when "1001" => data <= "1111110";
  when "1010" => data <= "1011111";
  when "1011" => data <= "1110011";
  when "1100" => data <= "0100111";
  when "1101" => data <= "1111001";
  when "1110" => data <= "1100111";
  when "1111" => data <= "1000111";
end case;
```



# Seven-Segment Decoder

```
type seven_segment is array (6 downto 0) ;
type rom_type is array (natural range <->) of seven_segment ;
constant hex_to_7 : rom_type (0 to 15) :=
( "0111111", -- 0
  "0011000", -- 1
  "1101101", -- 2
  "1111100", -- 3
  "1011010", -- 4
  "1110110", -- 5
  "1110111", -- 6
  "0011100", -- 7
  "1111111", -- 8
  "1111110", -- 9
  "1011111", -- A
  "1110011", -- B
  "0100111", -- C
  "1111001", -- D
  "1100111", -- E
  "1000111" ); -- F
```

Display segment index numbers :

```
  2
1  3
  6
0  4
  5
```

*-- Now, the ROM field can be accessed via a integer index*  
display\_bus <= hex\_to\_7 (i);



## PLA and ROM

### ■ ROM

- fixed input decoder Plane-as address
- all cased **case** statement

### ■ PLA

- Input allows don't care condition “-”, “x”
- Cannot use **case** statement
- Use Modeled ROM/PLA for large size design



## 2-Dimensional PLA

```
type std_logic_pla is array (natural range <>, natural range <>) of std_logic;
.....
procedure pla_table (
  constant invec : in std_logic_vector;
  signal  outvec : out std_logic_vector;
  constant table : in std_logic_pla
) is
  variable x : std_logic_vector (table'range(1)) ; -- product lines
  variable y : std_logic_vector (outvec'range) ; -- outputs
  variable b : std_logic ;
begin
  assert (invec'length + outvec'length = table'length(2))
  report "Size of Inputs and Outputs do not match table size"
  severity ERROR ;
```



## 2-Dimensional PLA (cont' ed)

*-- Calculate the AND plane*

x := (others=>'1');

for i in table'range(1) loop *-- PLA Table ROWs*

for j in invec'range loop

b := table(i,table'left(2)-invec'left+j);

if (b='1') then

x(i) := x(i) AND invec(j);

elsif (b='0') then

x(i) := x(i) AND NOT invec(j);

end if;

*-- If b is not '0' or '1' (e.g. '-') product line is insensitive to invec(j)*

end loop;

end loop;



## 2-Dimensional PLA (cont' ed)

*-- Calculate the OR plane*

y := (others=>'0');

for i in table'range(1) loop

for j in outvec'range loop

b := table(i,table'right(2) - outvec'right+j);

if (b='1') then

y(j) := y(j) OR x(i);

end if;

end loop;

end loop;

outvec <= y;

end pla\_table;



## 2-Dimensional PLA (cont' ed)


```
constant pos_of_fist_one : std_logic_pla (4 downto 0, 6 downto 0) :=  
  ( "1- - - 000", -- first '1' is at position 0  
    "01- - 001", -- first '1' is at position 1  
    "001- 010", -- first '1' is at position 2  
    "0001011", -- first '1' is at position 3  
    "0000111" ); -- There is no '1' in the input  
signal test_vector : std_logic_vector (3 downto 0);  
signal result_vector : std_logic_vector (2 downto 0);  
...  
-- Now use the pla table procedure with PLA pos_of_first_one  
-- test_vector is the input of the PLA, result_vector the output.  
...  
pla_table ( test_vector, result_vector, pos_of_fist_one );
```



## 2-Dimensional PLA Synthesis (1)

■ Altera 7000


Synthesis as glue logic

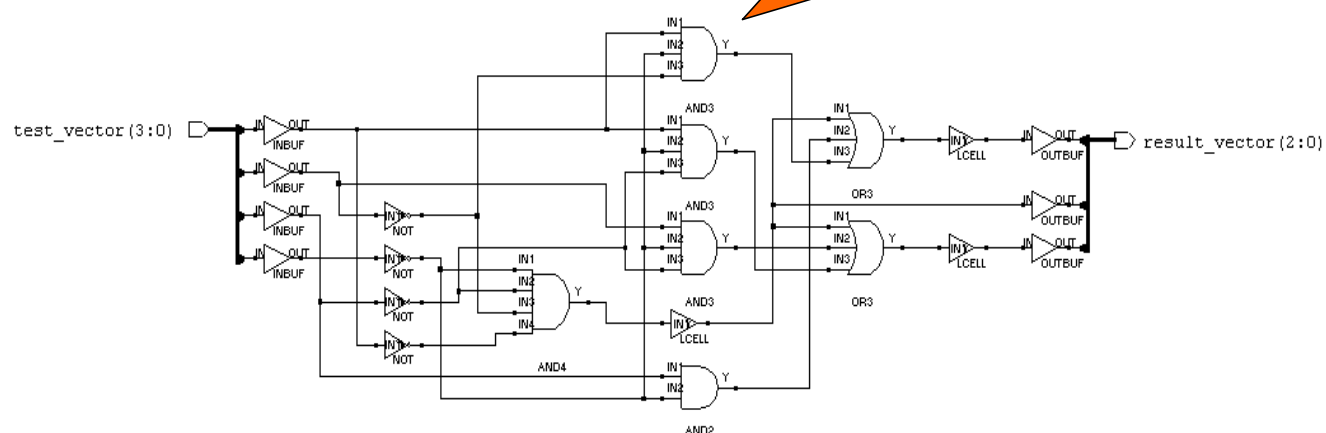

## 2-Dimensional PLA Synthesis (2)

■ Altera 10k

LUTs

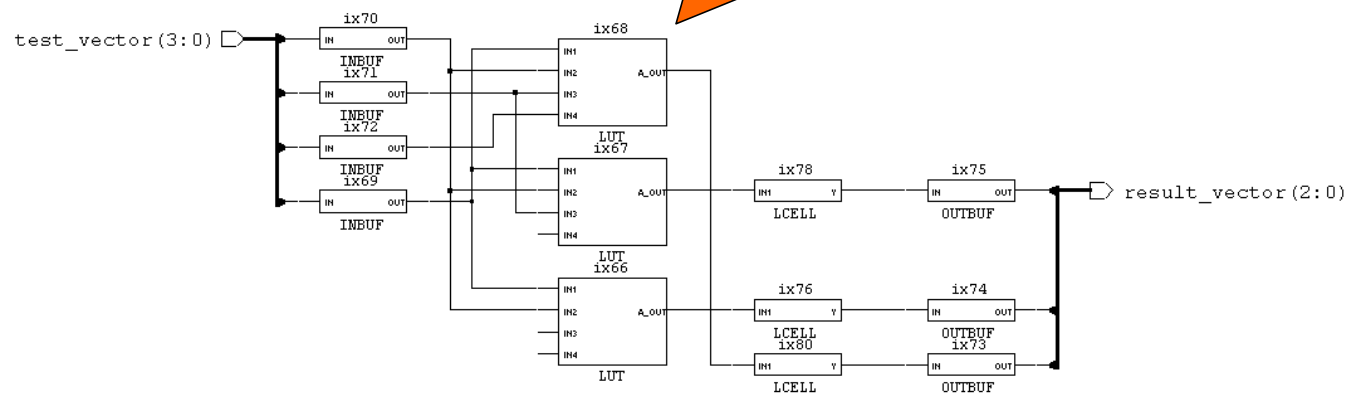

**a**NS Lab


**a**NS Lab

## Synthesis pitfalls

# Combinational Logic
 
## IF-ELSE Statement:

```
process (A,B,Sel)
begin
  if (Sel = '1') then
    O <= A;
  else
    O <= B;
  end if;
end process;
```




*No problem here, but...*

**a**NS Lab

# Combinational Logic (cont)
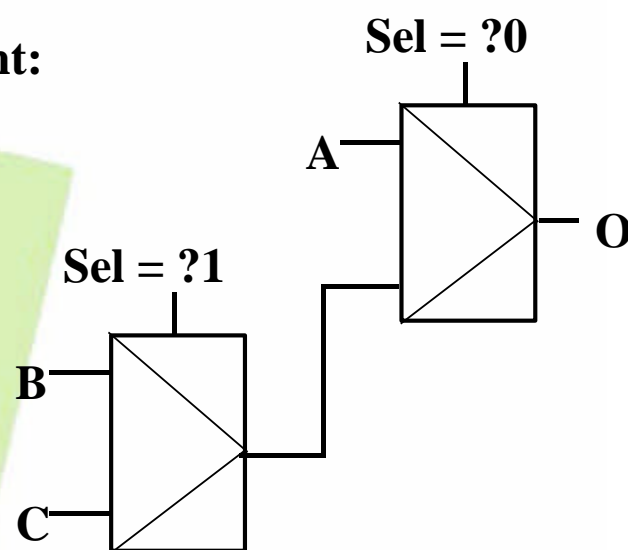
## IF-ELSIF-ELSE Statement:

```
process (A,B,C,Sel)
begin
  if (Sel = '00') then
    O <= A;
  elsif (Sel = '01') then
    O <= B;
  else
    O <= C;
  end if;
end process;
```




*Be careful with priorities!*

**a**NS Lab

## Combinational Logic (cont)
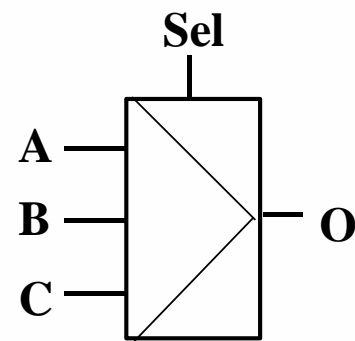
### ■ CASE Statement:

```
process (A,B,C,Sel)
begin
  case Sel is
    when '00' =>
      O <= A;
    when '01' =>
      O <= B;
    when others =>
      O <= C;
  end case;
end process;
```




*When in doubt, use a case statement!*

**a**NS Lab
 
## Accidental Latches

```
process (A,B,Sel)
begin
  if (Sel = '00') then
    O <= A;
  elsif (Sel = '10') then
    O <= B;
  end if;
end process;
```



*Don't leave out any conditions or you may get latches!*

**a**NS Lab



## Accidental Latches (cont)

architecture behavior of dff is

```
begin
  process(Rst,Clk)
  begin
    if Rst = '1' then
      Q1 <= (others=>'0');
    elsif rising_edge(Clk) then
      Q1 <= D1;
      Q2 <= D2; -- Note: should generate error
    end if;
  end process;
end behavior;
```

*Hint: what happens to Q2 when Rst is held high on a rising edge of Clk?*

**a**NS Lab

## Accidental Latches (cont)

```
process (current_state)
```

```
begin
```

```
  case current_state is
```

```
    when S0 =>
```

```
      O1 <= ?; O2 <= ?;
```

```
    when S1 =>
```

```
      O1 <= ?; O2 <= ?;
```

```
    when S2 =>
```

```
      O1 <= ?;
```

```
    when S3 =>
```

```
      O1 <= ?;
```

```
  end case;
```

```
end process;
```

*-- O2 doesn't matter in state S2 or S3*

**a**NS Lab

## Accidental Latches (cont)

```

process (current_state)
begin
    O2 <= ?; -- Be safe! Set default values here.
    case current_state is
        when S0 =>
            O1 <= ?; O2 <= ?;
        when S1 =>
            O1 <= ?; O2 <= ?;
        when S2 =>
            O1 <= ?; -- O2 doesn't matter in state S2 or S3
        when S3 =>
            O1 <= ?;
    end case;
end process;

```

**a**NS Lab

## Q & Qbar

```

ENTITY qqbar IS
PORT ( data, clk : IN std_logic;
      q,qbar : OUT std_logic );
END qqbar;

```

```



ARCHITECTURE a_qqbar OF qqbar IS
BEGIN
    PROCESS (data, clk)
    BEGIN
        IF clk='1' AND clk'EVENT THEN
            q <= data;
            qbar <= NOT q;
        END IF;
    END PROCESS;
END a_qqbar;

```

```

ARCHITECTURE a_qqbar_1 OF qqbar IS
BEGIN
    PROCESS (data, clk)
    BEGIN
        IF clk='1' AND clk'EVENT THEN
            q <= data;
        END IF;
    END PROCESS;
    qbar <= NOT q;
END a_qqbar_1;

```

  

**a**NS Lab

## Unsynthesizable Functions

```
function Vec_To_Int (INVEC : bit_vector) return integer is
  variable result: integer := 0;
begin
  for i in INVEC' reverse_range loop
    result := result * 2;
    if (INVEC(i) = '1') then
      result <= result + 1;
    end if;
  end loop;
  return result;
end Vec_To_Int;
```

*Theoretically synthesizable (check, it's just a wire) but you'll never get it through the synthesis tool!*



## UnSynthesizable VHDL

- After clauses (delay specifications)
- Initialization values
- Signals that have multiple clocks
- Unconstrained loops
- Text I/O (File types)
- Access types
- Real types (floating point numbers)



## Initialization Values

```
type state_type is (S0,S1,S2,S3,S4) ;  
signal current_state: state_type := S0 ;
```

- Simulation will start in state S0
- Synthesis will ignore initialization, so you get the device powerup for the initial state
- Summary: always provide a reset!



## Multiple Clocks

```
Process(clk0, clk1)  
begin  
  if clk0' EVENT and clk0=' 1' then  
    q <= d0;  
  elsif clk1' EVENT and clk1=' 1' then  
    q <= d1;  
  end if;  
end process;
```

```
Process(clk0)  
begin  
  if clk0' EVENT and clk0=' 1' then  
    q <= d0;  
  end if;  
end process;  
  
Process(clk1)  
begin  
  if clk1' EVENT and clk1=' 1' then  
    q <= d1;  
  end if;  
end process;
```

- Not synthesizable
- Rewrite with multiple registers



## Suggested Reading

---

- IEEE, *IEEE Standard 1076-1993 VHDL Language Reference Manual*
- IEEE, *IEEE Standard 1364 Verilog Language Reference Manual*
- Pellerin, David and Douglas Taylor, *VHDL Made Easy*, Prentice Hall, 1996
- Armstrong and Gray, *Structured logic Design with VHDL*, Prentice-Hall, 1996
- Internet: [comp.lang.vhdl](http://comp.lang.vhdl), [comp.lang.verilog](http://comp.lang.verilog), <http://www.vhdl.org>

